

一、FPGA 开发概述

- 理解 FPGA 的优势和开发流程
- 熟悉 Vivado 工作环境
- 清楚 Behavioral Simulation 和 IO planning 的作用

二、基本语法

数字声明（Number Specification）的方法，位宽、进制的表示方法。

<位宽>’ <进制> <数字> ， 例：4b’ 0011， 10’ hA3

位宽缺省 32 位，进制缺省十进制(二进制 b，十进制 d，八进制 o，十六进制 h)

其中位宽指的是转成二进制后的宽度，例如 10’ hA3 转成二进制后是

10’b00\_1010\_0011 (\_ 不能在第一位)

其中下划线\_是为了增强数字的可读性，可以放在除了第一位的任何一位。

这里十六进制数 3A 转成二进制数不满 10 位，所以最高的两位要补 0

如果是：6’ hA3，转成二进制是 6’ b10\_0011，最高的两位溢出舍弃

Verilog操作符

类型	符号	功能说明	类型	符号	功能说明
算术运算符 (双目运算符)	+	二进制加	关系运算符 (双目运算符)	>	大于
	-	二进制减		<	小于
	*	二进制乘		>=	大于或等于
	/	二进制除		<=	小于或等于
	%	求模		==	等于
位运算符 (除~是单目， 其余为双目运 算符)	~	按位取反	缩位运算符 (单目运算符)	!=	不等于
	&	按位与		&	缩位与
		按位或		~&	缩位与非
	^	按位异或			缩位或
	~~	按位同或		~	缩位或非
逻辑运算符 (除!是单目， 其余为双目运 算符)	或		移位运算符 (双目运算符)	~	缩位异或
				^	缩位同或
				~~ 或 ~~	
逻辑运算符 (除!是单目， 其余为双目运 算符)	!	逻辑非	移位运算符 (双目运算符)	>>	右移
	&&	逻辑与		<<	左移
		逻辑或			

位拼接运算符{ }

格式：

{信号 1 的某几位， 信号 2 的某几位， ...,信号 n 的某几位}

例：a=1， b=4'b1001， c=8'b11100110， d 为 6 位数，

d={a， b[1:0]， c[5:3]}= 6'b101100

变量的种类和声明方式

net 类型：主要是 wire 型 声明方式：wire < 位宽> 变量 1， 变量 2， ...

寄存器类型：主要是 reg 型 声明方式：reg < 位宽> 变量 1， 变量 2， ...

什么时候 reg 类型， 什么时候 wire 类型

连续赋值语句: assign a = 1’ b1; 这里的 a 必须是 wire 类型

过程赋值语句: b <= 1’ b1; 这里的必须是 reg 类型


输入输出缺省状态是 wire 类型

三、实例化调用 Instantiation

实例化调用时的语法格式： <module name> <instantiation name> port list

在一个模块中实例化引用另一个模块时的端口连接规则，什么情况下是 net 类型，什么情况下是 reg 类型，能够识别非法的端口连接和正确的端口连接。

在 port list 中为端口连接外部信号时，有顺序连接方法与按名字连接的方法

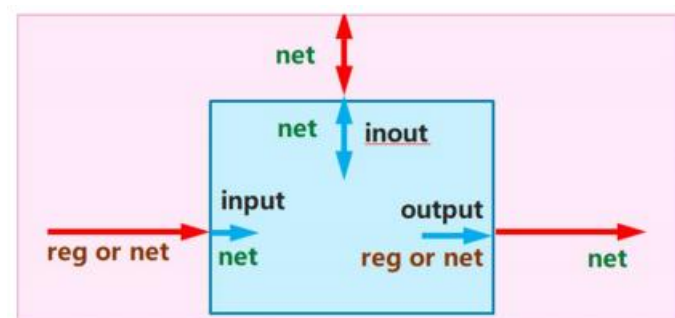


#### 四、组合逻辑电路设计

给定组合逻辑电路，能用三种建模方式来描述这个电路：

门级建模 Gate-level modeling: primitive (原语)

数据流建模 Dataflow Modeling: Continuous assignment (连续赋值语句 assign)

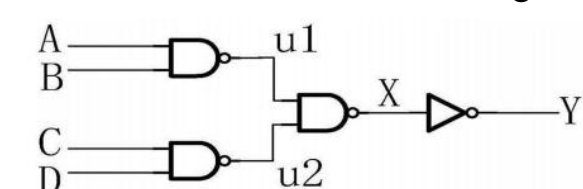行为级建模 Behavioral Modeling: Procedural block (过程块 always, initial)



熟记常用的 primitive;

使用 primitive 建模时，要注意 port list 的顺序：输出口在前，输入口在后，例：

nand r1 (u1, A, B); //这里的 r1 是实例名，使用原语时可省略

#### 五、时序逻辑电路设计

给出功能表，能根据功能表设计时序逻辑电路

如各种触发器 flip-flop (JK, D, T, ...), counter (Johnson, BCD, ...), shift register

注意 synchronous input 和 asynchronous input 的区别 (依赖时钟，不依赖时钟)，注意在 always 引导的过程块中如何表示这种区别。

能写 Testbench 验证所设计的 module


# // Review

--PLD→FPGA

--use FPGAs because

- speed up design process
- reduced cost
- increase design and operational efficiency
- reuse/adapted/upgraded because of programmability

## FPGA design flow

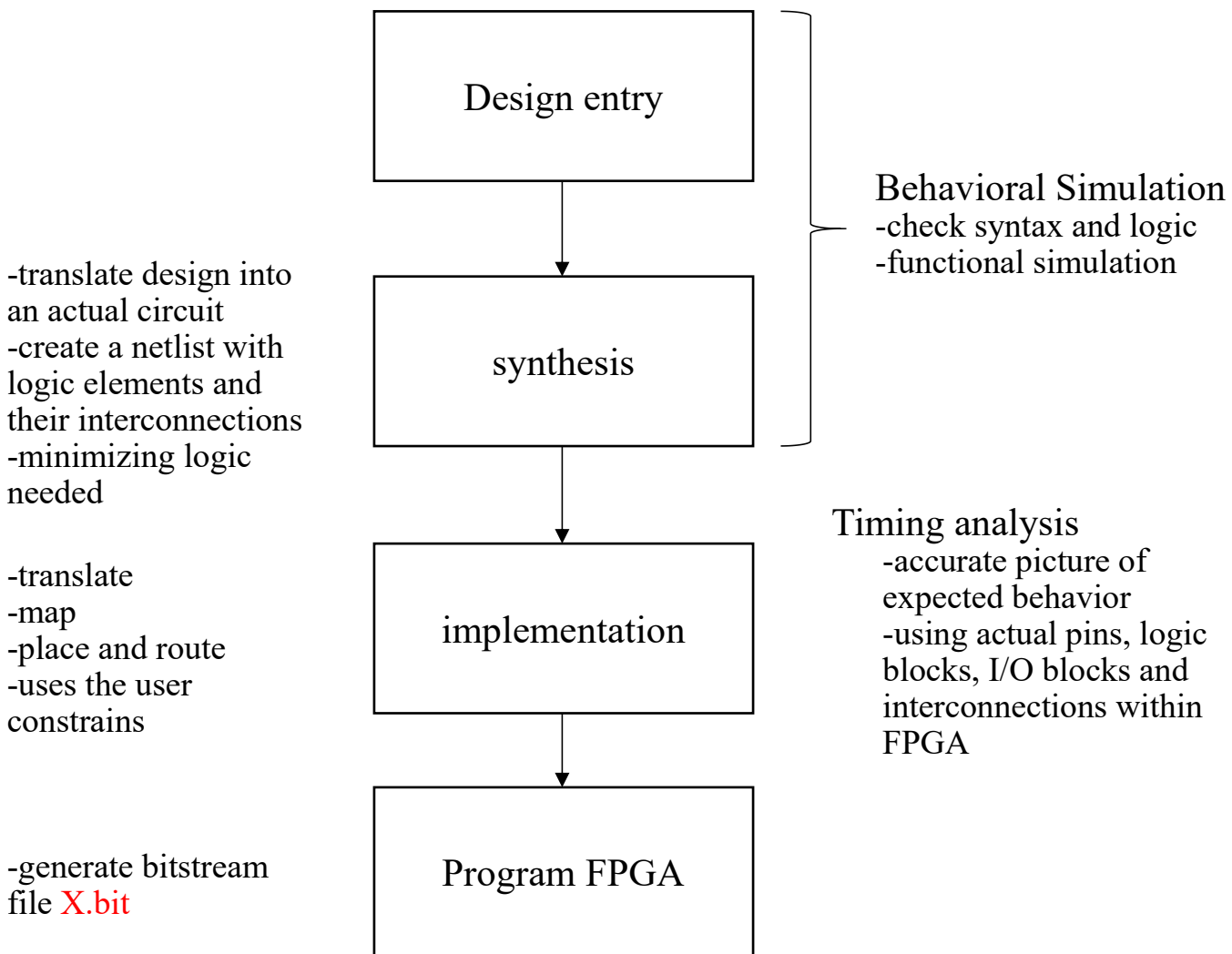

## C function

```
int main (          )
{
}
}
```

## Verilog Module

```
module main (          );

endmodule
```

## Verilog Syntax Classification

### --Definitions

-nets, registers, tasks, and functions

//nets and registers are common in use

//nets: wires, a way to transfer/transmit the value (logic 0/1)

//registers: data storage/memory

### --Declarative Code

-continuous assignments

-module (and primitive) instantiations

//declarative code describe the functionality and structure of system

//continuous assignments: to design combinational circuits- no storage; time-independent

### --Procedural Code

-initial and always blocks

//to describe the functionality of both combinational and sequential circuits-memory (from registers)

## Verilog nets

--Nets are used to connect model components together (like wires in a circuit)

**net\_type [range] [delay3] list\_of\_net\_identifiers;**

//[range]: [most significant code: most least code]

//[delay3]: propagation delay, non-synthesizable code, only for simulation

**wire w1, w2, w3;** //create 3 single bit wires named w1, w2, w3

**wire [7:0] w4, w5;** //create 2 8-bit wide wires named w4 and w5

**wire [31:0] #5 \_test;** /\*create 1 32-bit wide wire named \_test that is simulated with 5 units of propagation delay\*/

**reg [63:0] mem;** //create 1 64-bit register named mem

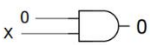

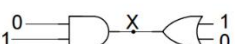
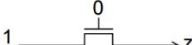
### --Net types

wire, tri, tri0, tri1, wand, wor, triand, trior, supply0, supply

### --Identifiers


Comprised of any number of letters, digits, "\_", and "\$"


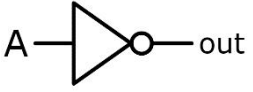




First character must be alphabetic or "\_"

0 :	
1 :	
X or x:	
Z or z :	

## Verilog Primitive Modeling

gate structure

AND		Y=A.B	
-----	---	-------	--

OR		$Y=A+B$	
NOT		$Y=A'$	
NAND		$Y=(A.B)'$	If at least one of the input is 0, then Y is '1'. Opposite to AND gate
NOR		$Y=(A+B)'$	If at least one of the input is 1, then Y is '0'. Opposite to OR gate
XOR		$Y=A \oplus B$ $=A'B+AB'$	When both inputs are same, the output is '0'.
XNOR		$Y=A \odot B$ $=AB+A'B'$	When both inputs are same, the output is '1'.

## Vivado

Design Sources (2)

Mux4 (Example1.v)

FullAdder (Example1.v)

- 2 modules within the file Example1.v
- top module: the module that will be synthesized
- Not top module: must make it top module in order to synthesize it (right-click and select the “set as top” option)

## Verilog Primitive Modeling

--prim instance\_name (out(s), in(s));

Vivado

2 modules within the file Example1.v

top module: the module will be synthesized

non-top module: must make it as the top module to synthesis it

## 3-input majority circuits

a	b	c	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1

1	1	0	1
1	1	1	1

$$X(\text{SOP}) = a'bc + ab'c + abc'$$

K-map:

c	0	1
ab		
00	0	0
01	0	1
11	1	1
10	0	1

$$X = ab + ac + bc$$

## Testbench Using Verilog

Verilog testbench properties

--contain a test module


-no I/O ports

-include registers to hold test values to input into the module being tested

-include wires to monitor the output(s) of the module being tested

✦ Synthesis successfully only means the code can be configured in hardware into the net list to fit into the FPGA, but Test can perform if it's functionally correct

## Tester

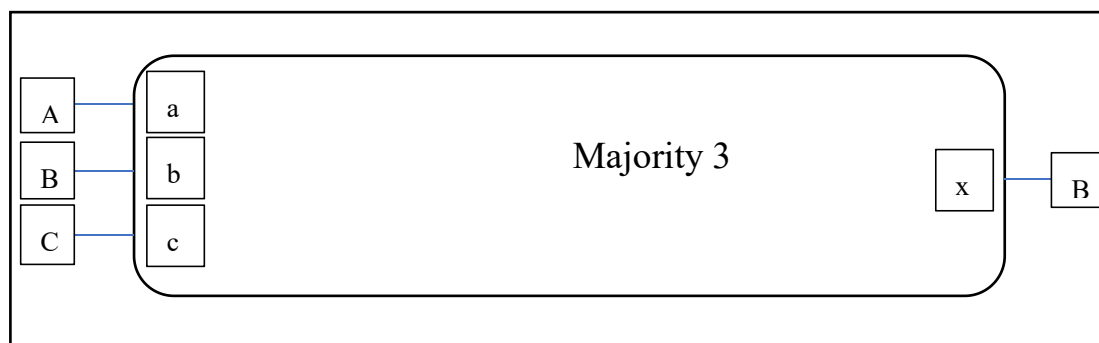

//A, B, C: registers

-used to provide input test values

//X: wire

-used for monitoring

-to perform testing of module, update the values stored in the input registers and read the resulting output values on the output wires

Primitive Modeling: realize a digital circuit using logic gate primitives

-require the circuit schematic

-describing physical structure of combinational circuit

Dataflow Modeling: realize a digital circuit using Boolean expressions

-require the Boolean expressions

-describing the functionality of complex combinational circuit

## Verilog Numbers

**number\_of\_bits'base\_identifier digits**

e.g.

4'd5 → 0101

8'b101 → 0000 0101

12'h58B\_3 → 0101 1011 0011 // '\_ ' is no sense, just for readable

12'Hxa → xxxxxxxx1010 // x means unknown

596 → 1001010100 /\*default base is decimal and numbers of the bits will match whatever is needed for the number\*/

2'hE → 4400 //11 would be truncated

wire [3:0] w1; /\*How to set w1 to 5? Take the w1=1010 as example. Number on that base is decimal, and w1=111110010(b). But w1 is only 4-bit, so w1=0010. \*/

/\* w1=5; don't use this format, use w1=4'd5 or w1=4'b0101. \*/

### Verilog Operators

Basic	OPERATION	DESCRIPTION	RESULT
Arithmetic	+ - * / %	Basic arithmetic	Multi-bit
Relational	> >= < <=	compare	One-bit

//% is modules, which is remainder from integer division.

// RESULT

e.g. 4'b1010+4'b0101→4'b1111

//4'b1010 and 4'b0101 are operands, and 4'b1111 is result

//multi-bit operands → multi-bit result

//result size will match operand size in most cases excepted it's set.

//Relations

//used in behavioral modeling

//Relation's result is 1 bit and the T is 1, while F is 0.

Equality	OPERATION	DESCRIPTION	RESULT
Logical	== !=	Equality not including Z, X	One-bit
Case	=== !==	Equality including Z, X	One-bit

//Logical is like relational and checking for equality, and the result is 1 bit and the T is 1, while F is 0.

//Case will compare the operands bit by bit. If the bases are different, the result must be F.

Boolean	OPERATION	DESCRIPTION	RESULT
Logical	<code>&amp;&amp;    !</code>	Simple logic	One-bit
Bit-wise	<code>~ &amp;   ^ ~</code> <code>~^</code>	Vector logic operation	One-bit
Reduction	<code>&amp; ~&amp;  ~  ^</code> <code>^~ ~^</code>	Perform operation on all bits	One-bit

*Bitwise operators and reduction operators are all represented by the same notation. The key to distinguishing these operators is the number of operands.*

//&& is AND, || is OR and ! is NOT.

If an operand is not 0 it is equivalent to logic 1. If an operand is equal to 0, it is equivalent to logical 0. If any of its bits are x or z, it's the same thing as x.

//~ is NOT, & is AND, | is OR, ^ is XOR, and ~^or~ is XNOR. They are for each operand bit.

//& is reduction AND, ~& is reduction NAND, | is reduction OR, ~| is reduction NOR, ^ is reduction XOR, and ^~or~ is reduction XNOR.

Reduction uses a single operand and the result is for whole operand.

//E.G.

**logical** `4'b0110 && 4'b0 →0(F)`

`4'b0110 || 4'b0 → 1(T)`

`4'b0110 && 4'b1000 → 1(T)`

`//any non-zero value is True(1)`

**bitwise** `~4'b0001 → 4'b1110`

`4'b1001 & 4'b0111 → 4'b0001`

`4'b1101 ^ 4'b0100 → 4'b1001`

**reduction** `&4'b1011 →1&0&1&1 →0(F)`

`&4'b1111 → 1&1&1&1 →1(T)`

`~|4'b1001 → 1|~0|~0|~1 →0(F)`

`^4'b1001 → 1^0^0^1 →0(F)`

Shift	OPERATION	DESCRIPTION	RESULT
Logical Right	<code>&gt;&gt;n</code>	Zero-fill Shift n places	Multi-bit
Logical Left	<code>&lt;&lt;n</code>	Zero-fill Shift n places	Multi-bit
Arithmetic Right	<code>&gt;&gt;&gt;n</code>		Multi-bit
Arithmetic Left	<code>&lt;&lt;&lt;n</code>		Multi-bit

//Logical shift's key is 0-fill shift n places.

**shifting** `4'b1001 <<1 → 4'b0010`

`4'b1001 <<3 → 4'b1000`

`4'b1101 >>1 → 4'b0110`



# Verilog Assignments

## Continuous assignments

**assign [delay3] list\_of\_net\_assignments;**

-Delay is propagation delay and for simulation only.

-Left-hand side of assignment must be a net.

-Continuous assign statements are not executed in source order.

E.G.

wire a, b, c;

① assign c=a/b;

② assign a=1'b1;

③ assign b=1'b0;

//Example: create a parity bit circuit(奇偶位电路)

TX(transmitter) → RX(receiver)

//8-bit data→provide error detection in the transmit and receive process using a parity bit

10101010

↓ 8-bit data

10101010\_ //‘\_’ is the parity bit

-set by TX and read by RX

-Even: set parity bit to a 1/0 so that the total number of 1s transmitted (data + parity bit) is even

-Odd: set parity bit to a 1/0 so that the total number of 1s transmitted (data + parity bit) is odd

//Back to the example, 10101010**1**→Odd, 10101010**0**→Even.

**1**01010101//transmitted with odd parity

↓

**0**01010101//receiver, count 4 1s which is even, therefore data is in error

//Traditional design process

1) Truth table with 8 inputs and parity bit outputs

2) Generate a Boolean expression

3) Minimize

data-in(8-bit)→Even Parity→data-out(9-bit)

-use reduction XOR operator to reduce 8-bit data to an Even Parity bit

XOR: 10101010→ $1^0 \wedge 1^0 \wedge 1^0 \wedge 1^0$ →**0(even parity bit)**

11100000→...→**1(even)**

**module Even Parity (data\_in, data\_out);**

**input [7:0] data\_in;**

**output [8:0] data\_out;**

**assign data\_out [8:1] =data\_in;**

**assign data\_out[0] ^=data\_in; //store parity bit into LSB**

**endmodule**

//Sometimes the parity bit is after the most significant bit, and sometimes it's before the least significant bit. It would be determined by the transmitter and receiver on how they place.

--EvenParity module testbench

**EvenParity UUT(.data\_in(d\_in),.data\_out(d\_out));**

// **EvenParity** is the module being instantiated.


// **UUT** is the instance name.

// **.date\_in/.date\_out** are port names from the module EvenParity.

// **d\_out/d\_in** are net names from the testbench.

// Above are dot notation to directly connect the ports.

### -Full Adder Example

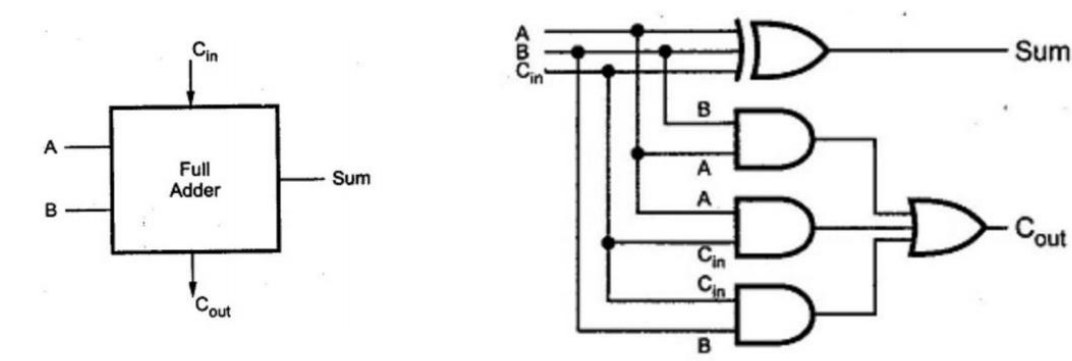

$A+B+C_{in} \rightarrow C_{out}+Sum$ , if A and B are n-bit wide, Sum is also wide.

If  $Sum=A+B+C_{in}$ , only capture the least significant m-bit and

$\{C_{out}, S\}=A+B+C_{in}$ ; //capture n+1 bits and store to Cout and S

//{} is concatenation operator.


//Cout is msb and S is lsb

A	B	C <sub>in</sub>	C <sub>out</sub>	S
0	0	0	0	0
1	0	0	0	1
0	1	0	0	1
1	1	0	1	0
0	0	1	0	1
1	0	1	1	0
0	1	1	1	0
1	1	1	1	1

n-nit wide. The result is (n+1)-bit

store to Sum.

### -4:1 Mux Example

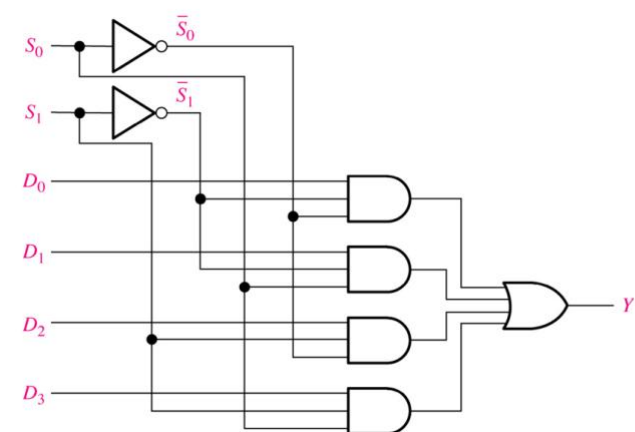

S1	S0	Y
0	0	
0	1	
1	0	
1	1	

$$Y=S1'S0'D0+S1'S0D1+S1S0'D2+S1S0D3$$

//use bitwise operators

**module Mux4\_DF(S,D,Y);**

**input [3:0] D;**

**input [1:0] S;**

**output Y;**

**assign Y=(~S[1]) & (~S[0]) & (D[0]) |**

**(~S[1]) & (S[0]) & (D[1]) |**

**(S[1]) & (~S[0]) & (D[2]) |**

**(S[1]) & (S[0]) & (D[3]);**

**endmodule**

## Behavioral Modeling

- Logic circuit described based on behavior of outputs with relation to the circuit inputs
  - Highest level of abstraction in Verilog modeling of logic circuits
  - Requires logic synthesis to create gate-level logic circuit
- Commonly used with sequential logic circuits
- Gate realization not needed prior to modeling

- just look at the behavior of the circuit

- highest level of abstraction

- Commonly used with sequential logic circuits

**reg [range] list\_of\_register\_identifiers;**

//reg: reg types

//[range]: [msb:lsb]

-procedural blocks //assign values to registers

-initial

**-always @ (sensitive/trigger list)**

-trigger on the change in level of a signal

**always @ (a)**

**always @ clr**

-always blocks triggered when a or clr change values, 0→1 or 1→0

-trigger on a specific edge of a signal

**always @ (posedge clk)**


**always @ (negedge clk)**

- always blocks triggered @ rising edge of 'clk' or falling edge of 'rst'

E.G.

-level change triggered

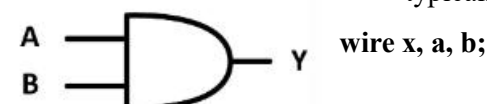-typically used to model combinational logic



**assign x=a&b;** //anytime the value of a or b changes, x is updated(continuously), the following is different

**wire a, b;**

**reg x;**

**always (a, b)** //anytime the value of a or b changes, the procedural block is executed(x is updated)


**begin**

**x=a&b;**

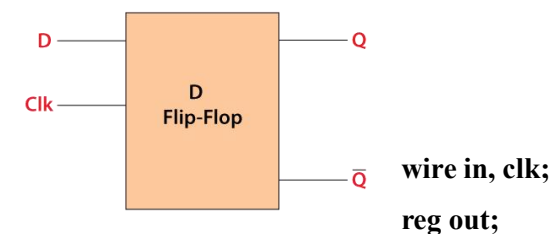**end**

-edge triggered

-typically used to model sequential logic




**always @ (posedge clk)** //state only updates on positive edge of clk signal, not when input changes

**begin**

**out=in;**

**end**

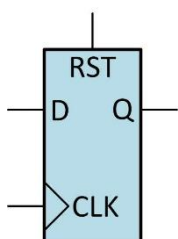

//RST: asynchronous reset, -logic low makes Q low

//read-list:<https://lambdageeks.com/d-flip-flop-circuit-working-truthtable-differences/>

**wire in, clk, rst;**

**reg out;**

**always @ (posedge clk, negedge rst)**

**begin**

**out= D & rst;**//rst fall, out=0

**end**

## Verilog Procedural Blocks

Only registers can be assigned within a procedural block.

-always: loops for continuous execution

-initial: execute only once at time zero, and it's by synthesizer

//Multiple procedural statements within the body of a procedural block must be bracketed by **begin** and **end** keywords. But when the

**begin – end** bracketing encloses only one procedural statement it is not mandatory.

-**initial** Statements

**initial begin**

```

clk = 0;
reset = 0;
req_0 = 0;
req_1 = 0;

```

**end**

//**clk**, **reset**, **req\_0**, and **req\_1** are all registers.

//**initial** means at time 0, all values are 0.

- always assignment

- An **always** block should have a **sensitive list**(**trigger**) or a delay associated with it
- The sensitive list tells the always block when to execute the block of code
- The **@** symbol after **always** indicates that the block will be triggered "at" the condition in parenthesis

Procedural **blocking** assignments (=)

-not executed by FPGA, but by Vivado during synthesis into hardware

-A blocking assignment uses a reg data type on the left-hand side and an expression on the right-hand side of an equal sign


-May contain intra-assignment delay or event control

E.G. Blocking (=)

```

...
initial begin:
b=1;
#100; //delay
b=#80 0;
b=#120 1;
...

```

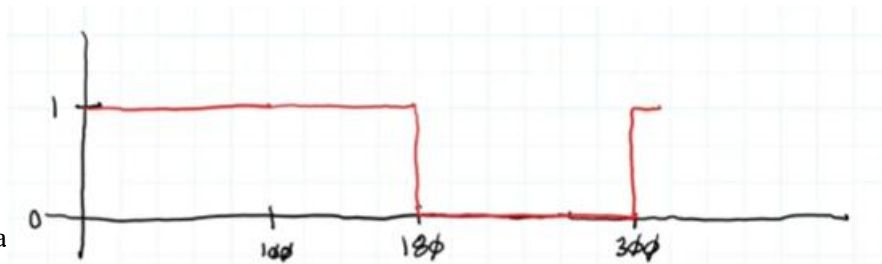

Procedural **nonblocking** a

-When flow reaches a non-blocking assignment, the right-hand side of the assignment is evaluated and will be scheduled for the left-hand side reg to take place when the intra-assignment control is satisfied

E.G. nonblocking

```

...
initial begin:
a<=1;
#100; //delay
a<=#80 0;
a<=#120 1; //start at sa
...

```



E.G.

**reg A, B;**

**initial**

**begin**

**A=0**

**end**

**always @ (posedge clk)**

```

begin
    A=~A;
    B=A;
end //A=1,B=1
or

```

```

reg A, B;
initial
begin
    A=0

```

end

always @ (posedge clk)

begin

```

    A<=~A;

```

```

    B<=A;


```

```


end //A=1,B=0

```

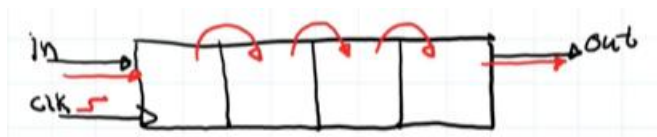//5-bit serial-in serial-out shift register



NON-BLOCKING

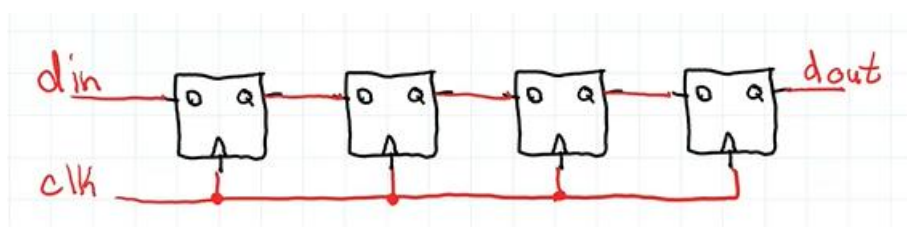

```

module SR4_NB(din, dout, clk); //4-bit shift register non-blocking

```

```

input din, clk;

```

```

output dout;

```

```

reg [3:0] Q;

```

```

always @ (posedge clk) //model the shifting within the shift register

```

```

begin

```

```

    Q [0] <=din;//serial inputs

```

```

    Q [1] <=Q [0];

```

```

    Q [2] <=Q [1];


```

```

    Q [3] <=Q [2];

```



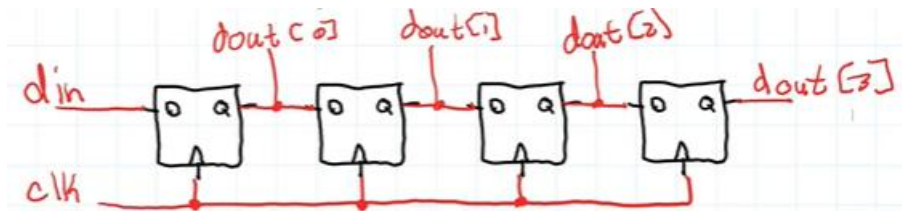

```

module SR4_NB(din, dout, clk); //4-bit shift register non-blocking
input din, clk;
output [3:0] dout;
reg [3:0] Q;
always @ (posedge clk) //model the shifting within the shift register
begin
    Q[0]<=din;//serial inputs
    Q[1]<=Q[0];
    Q[2]<=Q[1];
    Q[3]<=Q[2];
end
assign dout=Q; //serial output updates when Q[3] value changes
endmodule

```

//Tester

```

module Tester();//testbench to test the non-blocking SR4
reg din, clk;
wire [3:0] dout;
SR4_NB UUT (.din(din), .clk(clk), .dout(dout));
initial
begin
    clk=1'b0;
    din=1'b1;
    #5;
    clk=~clk;
    #5;
    clk=~clk;
    #5;
    clk=~clk;
    #5;
    clk=~clk;
    #5;
    clk=~clk;
    #5;
    clk=~clk;

```



```

#5;
clk=~clk;

#5;
clk=~clk;

#5;
clk=~clk;

end

endmodule

```



-initialize shift register

```

module SR4_NB(din, dout, clk); //4-bit shift register non-blocking

```

```

input din, clk;

```

```

output [3:0] dout;

```

```

reg [3:0] Q;

```

```

initial

```

```

begin

```

```

Q=4'b0; //initialize shift register to be clear

```

```

end

```

```

always @ (posedge clk) //model the shifting within the shift register

```

```

begin

```

```

    Q[0]<=din; //serial inputs

```

```

    Q[1]<=Q[0];

```

```

    Q[2]<=Q[1];

```

```

    Q[3]<=Q[2];

```

```

end

```

```

assign dout=Q; //serial output updates when Q[3] value changes


```

```


endmodule

```

//Tester is as same as the second

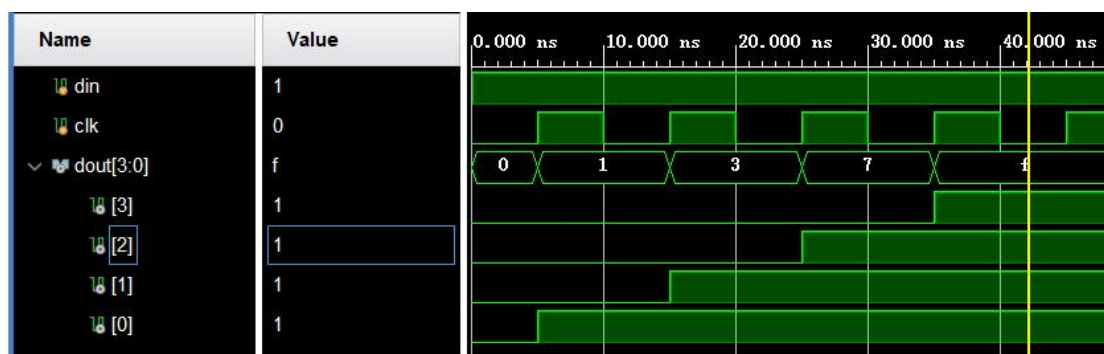

## Blocking

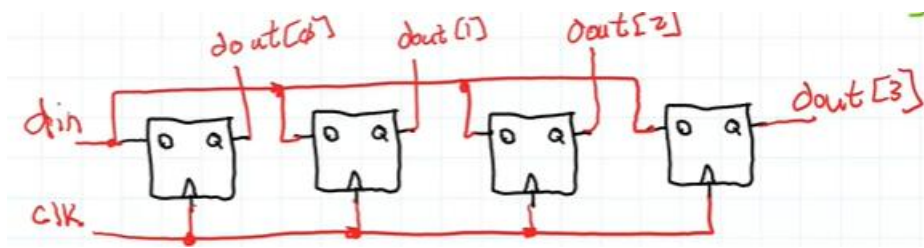

```

module SR4_B(din, dout, clk); //4-bit shift register non-blocking
input din, clk;
output [3:0] dout;
reg [3:0] Q;
initial
begin
Q=4'b0; //initialize shift register to be clear
end
always @ (posedge clk) //model the shifting within the shift register
begin
    Q[0]=din; //serial inputs
    Q[1]=Q[0];
    Q[2]=Q[1];
    Q[3]=Q[2];
end
assign dout=Q; //serial output updates when Q[3] value changes
endmodule

```

//Tester


```

module Tester();//testbench to test the non-blocking SR4
reg din, clk;
wire [3:0] dout, dout2;
SR4_NB UUT (.din(din), .clk(clk), .dout(dout));
SR4_B UUT2 (.din(din), .clk(clk), .dout(dout2));
initial
begin
clk=1'b0;


```

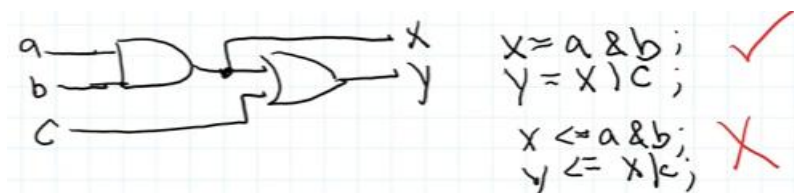**endmodule**

--combinational circuits→blocking assignments



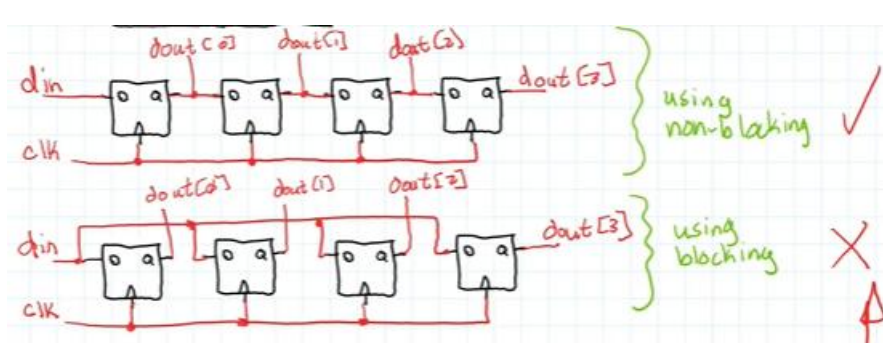--sequential circuits→non-blocking assignments



-If several assignments appear at the same real time in a procedural body, the last assignment overrides all others.

-If program flow in **two procedural bodies reaches assignments to the same reg at exactly the same time** (multi-sources/race condition, **which should be avoid**), the outcome of the value assigned to the left-hand side of the assignment will not be known.

-use **always** to Test

**module Tester();**//testbench to test the non-blocking SR4

**reg** din, clk;

**wire** [3:0] dout, dout2;

SR4\_NB UUT (.din(din), .clk(clk), .dout(dout));

SR4\_B UUT2 (.din(din), .clk(clk), .dout(dout2));

**initial**

**begin**

    clk=1'b0;

    din=1'b1;

**end**

**always**//run continuously to generate clock signal


**begin**

    clk=~clk;

    #5;

**end**

**endmodule**

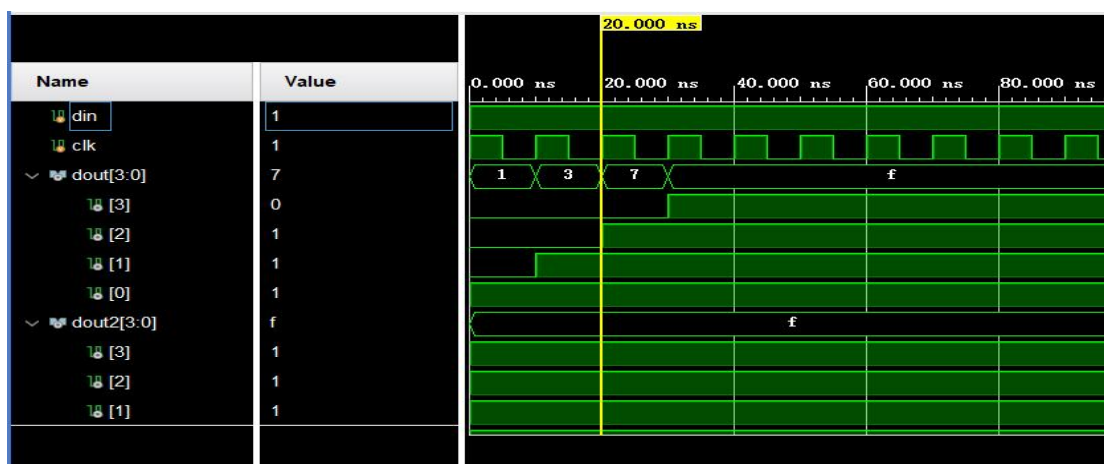

-reduce the chance of race

module Tester();//testbench to test the non-blocking SR4

reg din, clk;

wire [3:0] dout, dout2;

SR4\_NB UUT (.din(din), .clk(clk), .dout(dout));

SR4\_B UUT2 (.din(din), .clk(clk), .dout(dout2));

initial

begin

clk=1'b0;

din=1'b1;

end

always//run continuously to generate clock signal


begin

#5;

clk=~clk;

end

endmodule

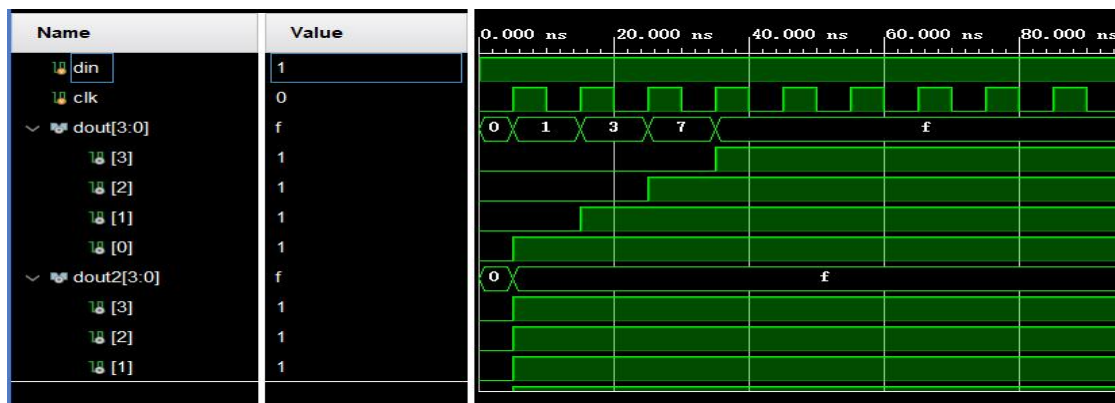

## Verilog Conditional Statements

- Procedural conditional ( ? ) operator


-Compact single-way conditional expression

**test ? true\_expression : false\_expression**

e.g.

**wire [3:0] a, b, max;**

**assign max=(a>b) ? a:b;**

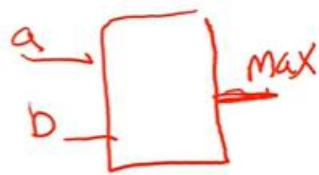

- Procedural if – else – else if statements

-if part of statement only taken for conditions equal

-Use of begin-end bracketing is **optional** (if only 1 statement)

-The else if statement is really a nested if statement within the original else statement

-In coding combinational circuits, it is recommended that the last else of a group of nested if-else statements appears without an

if

//2-bit mux example

```
module mux2 (S, din, dout);
```

```
input S;
```

```
input [1:0] din;
```

```
output dout;
```

```
reg dout; // or output reg dout;
```

```
always @ (S, din) //S and din are inputs
```

```
begin
```

```
if (S==1'b0) //use == to justify equal or not
```

```
begin
```

```
dout=din[0];
```

```
end
```

```
else
```


```
begin
```

```
dout=din[1]; //use blocking assignments for combinational logic
```

```
end
```

```
end
```

```
endmodule
```

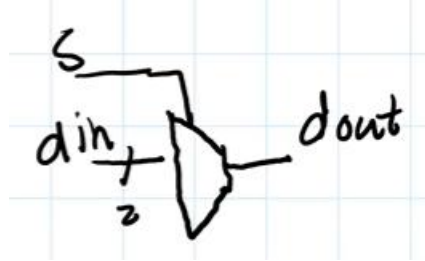

- Procedural case statement

- Convenient multi-way selection statement

- Compares an expression to a series of cases and executes the statement or statement group associated with the first matching case

**case** (expression)

```
case1: statement;
```

```
case2: statement;
```

```
...
```

```
default: statement;
```

```
endcase
```

//2-bit mux example

```
module mux2 (S, din, dout);
```

```
input S;
```

```
input [1:0] din;
```

```
output reg dout;
```

```
always @ (S, din)
```

```
begin
```

```
case(S)
```


```
1'b0: dout=din [0];
```

```
1'b1: dout=din [1];
```

```
default: dout=0;
```

```
endcase
```

```
end
```

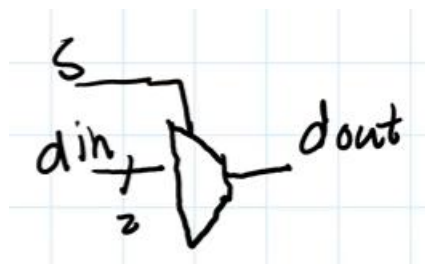

endmodule

# Verilog Iterative Statements

## Verilog Loops

-use to replicate hardware //make copies of the hardware

-control variable //often integer numbers

1.initialled

2.test

-Verilog requires all loops to have a fixed number of iterations

3.updated

-Verilog does not have auto increment/decrement operators like C ( ++/-- )

### • Procedural **for** statement

-Used for indexed looping

**for (init\_assignment; constant expression; step)**

**begin**


... // statements to repeat

**end**


// **constant expression** is test and **step** is updated

-Can be nested or combined with other procedural statements

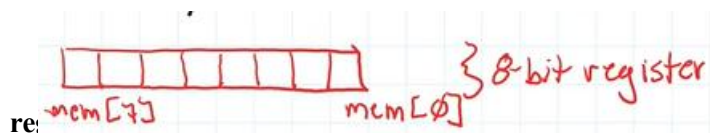-use for loop to initialize a memory element



**mem = 8'b0;** //initialize reg to 0

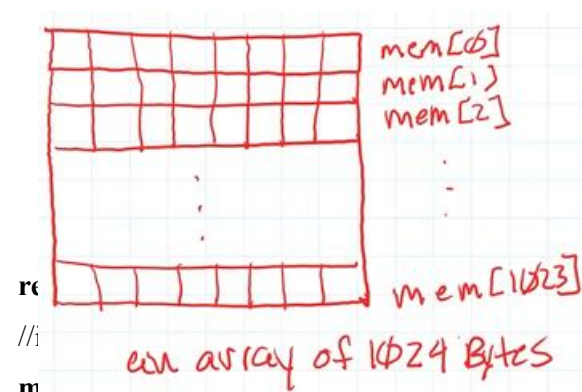

**mem[1] = 8'b0;**

**mem[2] = 8'b0;**

...

```
mem[1023] = 8'b0;
```

```
integer cnt;
```

```
initial
```

```
begin
```

```
    for (cnt=0; cnt<1024; cnt=cnt+1)
```

```
    begin
```

```
        mem[cnt]=8'b0;
```

```
    end
```

- Procedural **while** statement

-Executes as long as a conditional expression evaluates as true

```
while ( conditional_expression )
```

```
begin
```

```
    ... // statements to repeat
```

```
end
```

e.g.

```
for (cnt=0; cnt<1024; cnt=cnt+1)
```

```
begin
```

```
    mem[cnt]=8'b0;
```

```
end
```

can be turned into

```
cnt=0; //initialize control variable
```

```
while(cnt<1024) //test control variable
```

```
begin
```


```
    mem[cnt]=8'b0;
```

```
    cnt=cnt+1; //update control variable
```

```
end
```

## Verilog Behavioral Modeling Applications

— 3-to-8 address decoder

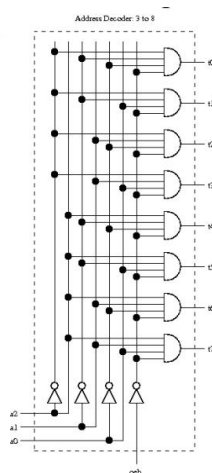

r@udavton.edu

a0, a1, a2: binary address to memory location, allows to select which line of the memory to access



oeb: output to function as a decoding of the input when oeb=0 to enable

//3-to-8 address decoder in Verilog

1) implement with case statement

```
module decoder_38( in_data, oeb, out_data);
```

```
input wire [2:0] in_data;
```

```
input oeb;
```

```
output reg [7:0] out_data;
```

```
always @(in_data,oeb)
```

```
begin
```

```
    if(oeb==1'b0)
```

```
    begin
```

```
        case(in_data)
```

```
            3'b000: out_data=8'b0000_0001;
```

```
            3'b001: out_data=8'b0000_0010;
```

```
            3'b010: out_data=8'b0000_0100;
```

```
            3'b011: out_data=8'b0000_1000;
```

```
            3'b100: out_data=8'b0001_0000;
```

```
            3'b101: out_data=8'b0010_0000;
```

```
            3'b110: out_data=8'b0100_0000;
```

```
            3'b111: out_data=8'b1000_0000;
```

```
            default:out_data=8'b0000_0000;
```

```
        endcase
```

```
    end
```

```
    else
```

```
    begin
```

```
        out_data=8'b0000_0000;
```

```
    end
```

```
end
```

```
endmodule
```

2) implement with shift operation

000→8'b0000\_0001

010→8'b0000\_0100

8'b0000\_0001<<010→8'b0000\_0100

```
module decoder_38( in_data, oeb, out_data);
```

```
input wire [2:0] in_data;
```

```
input oeb;
```

```
output [7:0] out_data;
```

```
//use continuous assignment
```

```
assign out_data=(oeb==1'b0) ? (8'b0000_0001<<in_data):(8'b0000_0000);
```

```
endmodule
```

3) implement with a for loop



```
-set out_data [in_data] = 1'b1;

//set each bit of out_data based upon in_data

module decoder_38( in_data, oeb, out_data);
input wire [2:0] in_data;
input oeb;
output [7:0] out_data;
reg [7:0] out_data;
integer cnt;
always @( in_data, oeb)
begin
    if (oeb ==1'b0)//output is enabled
    begin
        for(cnt=0; cnt<8; cnt=cnt+1) //set the value for each bit of the output
        begin
            if(cnt==in_data) //check if current bit location equals to the input value
            begin
                out_data[cnt]=1'b1;
            end
            else
            begin
                out_data[cnt]=1'b0;
            end
        end
    end
end
endmodule
```

Combinational logic circuit examples



4-bit comparator

  

COMPARING INPUTS				CASCADING INPUTS			OUTPUTS		
A3, B3	A2, B2	A1, B1	A0, B0	A > B	A < B	A = B	A > B	A < B	A = B
A3 > B3	X	X	X	X	X	X	H	L	L
A3 < B3	X	X	X	X	X	X	L	H	L
A3 = B3	A2 > B2	X	X	X	X	X	H	L	L
A3 = B3	A2 < B2	X	X	X	X	X	L	H	L
A3 = B3	A2 = B2	A1 > B1	X	X	X	X	H	L	L
A3 = B3	A2 = B2	A1 < B1	X	X	X	X	L	H	L
A2 = B3	A2 = B2	A1 = B1	A0 > B0	X	X	X	H	L	L
A3 = B3	A2 = B2	A1 = B1	A0 < B0	X	X	X	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	H	L	L	H	L	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	L	H	L	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	X	X	H	L	L	H
A3 = B3	A2 = B2	A1 = B1	A0 = B0	H	H	L	L	L	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	L	L	L	H	H	L

//logic block diagram, the actual circuit, truth table

4-bit comparator

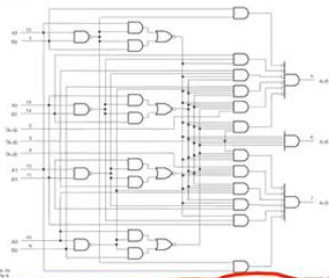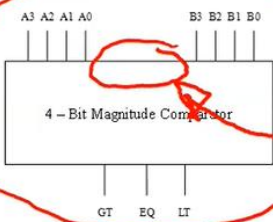

COMPARING INPUTS				CASCADING INPUTS			OUTPUTS		
A3, B3	A2, B2	A1, B1	A0, B0	A > B	A < B	A = B	A > B	A < B	A = B
A3 > B3	X	X	X	X	X	X	H	L	L
A3 < B3	X	X	X	X	X	X	L	H	L
A3 = B3	A2 > B2	X	X	X	X	X	H	L	L
A3 = B3	A2 < B2	X	X	X	X	X	L	H	L
A3 = B3	A2 = B2	A1 > B1	X	X	X	X	H	L	L
A3 = B3	A2 = B2	A1 < B1	X	X	X	X	L	H	L
A2 = B3	A2 = B2	A1 = B1	A0 > B0	X	X	X	H	L	L
A3 = B3	A2 = B2	A1 = B1	A0 < B0	X	X	X	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	H	L	L	H	L	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	L	H	L	L	H	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	X	X	H	L	L	H
A3 = B3	A2 = B2	A1 = B1	A0 = B0	H	H	L	L	L	L
A3 = B3	A2 = B2	A1 = B1	A0 = B0	L	L	L	H	H	L

```
module comp4 (A, B, iAltB, iAeqB, iAgtB, oAltB, oAeqB, oAgtB);
input [3:0] A,B;
input iAltB, iAeqB, iAgtB;
output reg oAltB, oAeqB, oAgtB;
always @ (A, B, iAltB, iAeqB, iAgtB)
begin
    //reset all output regs
    oAltB=1'b0;
    oAeqB=1'b0;
```

```

oAgtB=1'b0;
if(A>B)
begin
    oAgtB=1'b1;
end
else if (A<B)
begin
    oAltB=1'b1;
end
else if (A==B)
begin
    //check cascading input
    case({iAgtB, iAltB, iAeqB})
        3'b100: oAgtB=1'b1;
        3'b010: oAltB=1'b1;
        3'b001: oAeqB=1'b1;
        3'b000: begin
            oAgtB=1'b1;
            oAltB=1'b1;
        end
        default:
            begin
                oAgtB=1'b0;
                oAltB=1'b0;
                oAeqB=1'b0;
            end
    endcase
end
end
endmodule

```

-Vivado Synthesis Warning

-inferring latch for variables xxx register

//latch: maintain values

-caused when a registered is updated within a conditional expression inside a procedural block, but the register is not updated in all branches of the conditional

- Coding pitfalls

-Assigning a variable within multiple procedure blocks

//Race condition → non-deterministic operations

-Forgetting to include all inputs in sensitivity list

//Use of implicit sensitivity lists **always @ (\*)**

- Warning: Failure to assign all controlled outputs on every  
//iteration of a procedural block (inferred latch)
- Error: Failure to use a constant iteration count results  
//in an unsynthesizable code (for / while)

## Structural Modeling

- Digital system (logic circuit) described using **instantiation** of one or more design modules
  - Built-in primitives
  - Dataflow models
  - Behavioral models
- Focuses on **interconnections** between lower-level design modules
- Requires logic synthesis to create gate-level logic circuit


top module:

- ① instantiation
- ② interconnections

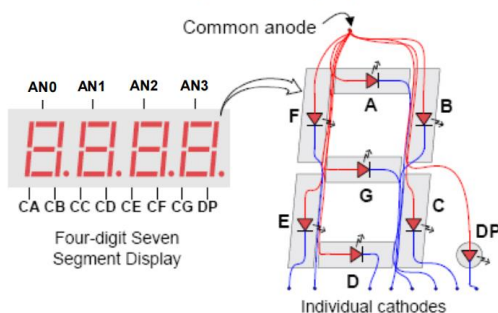
## Module Instantiation

- A module may be composed of instances of other modules
- The full hierarchical path name of each module specifies its location in the hierarchy
- Only top level module is instantiated by its module definition

- Decoder Example
  - Develop a decoder to translate a 4-bit hexadecimal number to a seven segment display



x	a	b	c	d	e	f	g
0	0	0	0	0	0	0	1
1	1	0	0	1	1	1	1
2	0	0	1	0	0	1	0
3	0	0	0	0	1	1	0
4	1	0	0	1	1	0	0
5	0	1	0	0	1	0	0
6	0	1	0	0	0	0	0
7	0	0	0	1	1	1	1
8	0	0	0	0	0	0	0
9	0	0	0	0	1	0	0
A	0	0	0	1	0	0	0
B	1	1	0	0	0	0	0
C	0	1	1	0	0	0	1
D	1	0	0	0	0	1	0
E	0	1	1	0	0	0	0
F	0	1	1	1	0	0	0

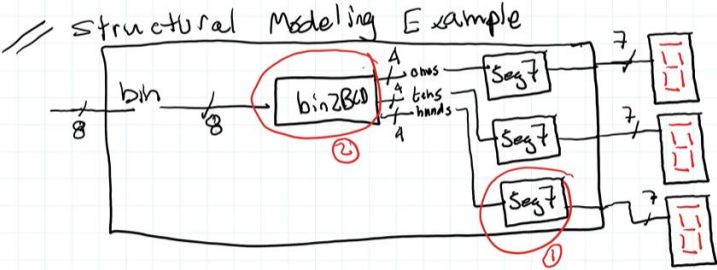


-Seg 7 module

BCD value

LSB

MSB

x	a	b	c	d	e	f	g
0	0	0	0	0	0	0	1
1	1	0	0	1	1	1	1
2	0	0	1	0	0	1	0
3	0	0	0	0	1	1	0
4	1	0	0	1	1	0	0
5	0	1	0	0	1	0	0
6	0	1	0	0	0	0	0
7	0	0	0	1	1	1	1
8	0	0	0	0	0	0	0
9	0	0	0	0	1	0	0

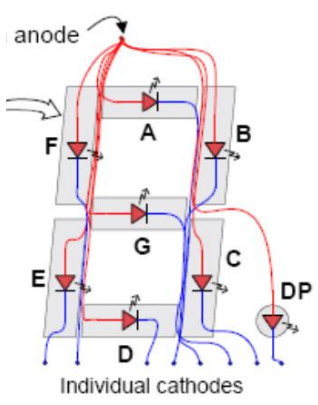

0=on, 1=off

-Bin2BCD module


-shift and add 3 methods

- ① shift binary value left 1 bit into BCD bits
  - ② if any BCD digital is  $\geq 5$ , then add 3 to the digit
- :repeat 8 times to get 8-bit input into BCD outputs

BCD outputs

	hundreds	tens	ones	binary number input
desired result	0010	0101	0101	1111 1111 (255)
S1			1	111 1111
S2			11	11 11110
S3			725 (111)	1 111100
+3			1010	1111000
S4		1	0101	111 0000
+3		1	1000	111 0000
S5		625 11	0001	110 0000
S6		110	0011	1100 0000
+3		1001	0011	1100 0000
S7	1	0010	0111	1 000 0000
+3	1	0010	1010	1 000 0000
S8	10	0101	0101	0000 0000

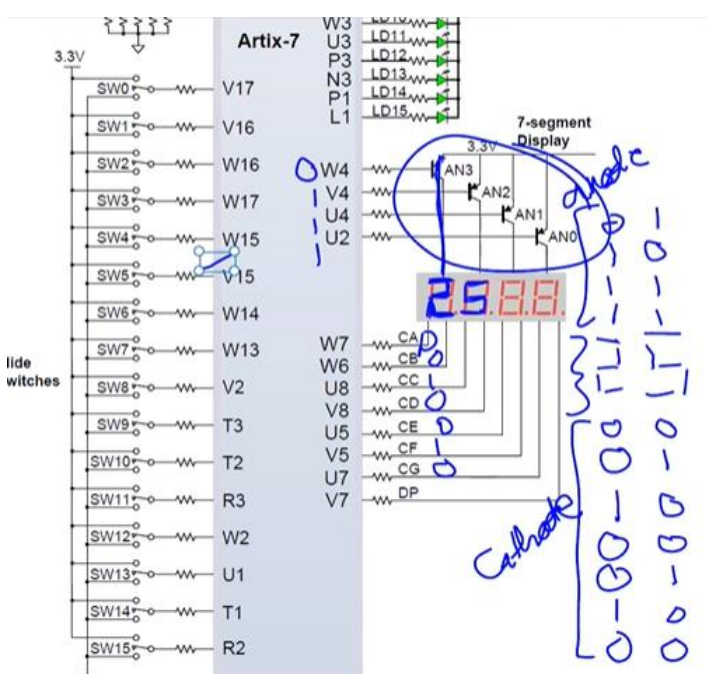do not check BCD digits if  $\geq 5$  after shift + 8



anode: 阴极,

0=number on,


1=number off

cathode: 阳极;

0=segment on,

30

1=segment off

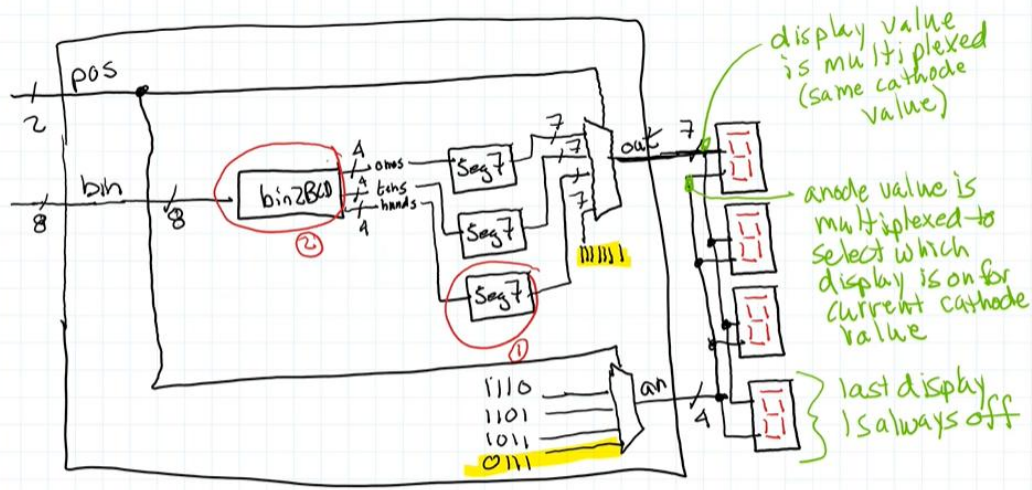

```

module top(pos, bin, out, an);
input [1:0] pos;
input [7:0] bin;
output reg [6:0] out;
output reg [3:0] an;
wire [3:0] ones, tens, hunds;
wire [6:0] seg7ones, seg7tens, seg7hunds;
bin2BCD U1 (.bin(bin), .ones(ones), .tens(tens), .hunds(hunds));
Seg7 U2 (.BCD(ones),.out(seg7ones));
Seg7 U3 (.BCD(tens),.out(seg7tens));
Seg7 U4 (.BCD(hunds),.out(seg7hunds));
always @ (pos,seg7ones, seg7tens, seg7hunds)
begin
//implement mux for 7 segment display
case(pos)
2'b00://ones
begin
out=seg7ones;
an=4'b1110;
end
2'b01://tens
begin
out=seg7tens;
an=4'b1101;
end
2'b10://hunds
begin
out=seg7hunds;
an=4'b1011;
end
endcase
end

```

```

        end
    2'b11://thousands
    begin
        out=7'b1111111;
        an=4'b0111;
    end
endcase
end
endmodule

module bin2BCD(bin, ones, tens, hunds);
input [7:0] bin;
output [3:0] ones, tens, hunds;
reg [19:0] temp; //temporary register to hold 8-bit binary input and BCD output during shifting and add 3 process
integer cnt; //control variable for the for loop
always @(bin)
begin
    temp={12'b0, bin}; //concatenate 12 bits of 0 with binary input and store to temp register
    //perform the shift and add 3 algorithm 8 times
    for (cnt=0; cnt<8; cnt=cnt+1)
    begin
        temp = temp << 1;//shift temp register to left by 1
        if(cnt<7)//first shifts
        begin
            //test each BCD output >=5
            if(temp[11:8]>=5)//if ones digit >=5
            begin
                temp[11:8]=temp[11:8]+3;
            end
            if(temp[15:12]>=5)//if tens digit >=5
            begin
                temp[15:12]=temp[15:12]+3;
            end
            if(temp[19:16]>=5)//if hunds digit >=5
            begin
                temp[19:16]=temp[19:16]+3;
            end
        end
    end
end
end
end

```



```

assign ones=temp[11:8];
assign tens=temp[15:12];
assign hunds=temp[19:16];
endmodule

```

```


module Seg7 (BCD, out);
input [3:0] BCD;
output reg [6:0] out;
always @ (BCD)
begin
    case(BCD) //care about the lsb and msb
        4'b0000:out=7'b1000000;
        4'b0001:out=7'b1111001;
        4'b0010:out=7'b0100100;
        4'b0011:out=7'b0110000;
        4'b0100:out=7'b0011001;
        4'b0101:out=7'b0010010;
        4'b0110:out=7'b0000010;
        4'b0111:out=7'b1111000;
        4'b1000:out=7'b0000000;
        4'b1001:out=7'b0010000;
        default: out=7'b1111111; //turn off display if invalid number
    endcase
end
endmodule

```

## Sequential Circuit Applications
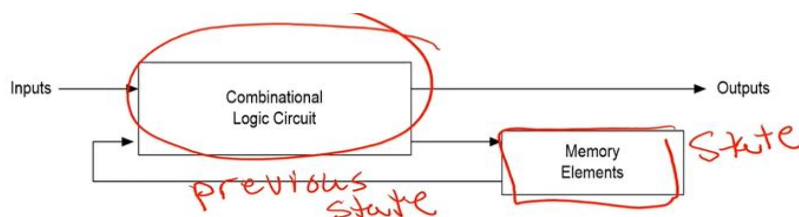
### Sequential Circuits

- Contain both combinational logic and memory elements
  - Flip-flops
  - Shift registers
  - Counters



## Flip Flops

- Asynchronous Flip-flop Inputs
  - Inputs that affect the state of the flip-flop independently of the clock signal
  - Preset (PRE)
    - Places the flip-flop into the SET state
  - Clear (CLR)
    - Places the flip-flop into the RESET state
  - Must be included within **always** block sensitivity list

### Sequential Circuits Examples

D flip-flop with asynchronous PRE and CLR

PRE: set state =1. CLR: set state =0

```
module DFF (clk, D, clr, pre, Q, Qnot);// clr, pre are active high
```

```
input clk, D, clr, pre;
```

```
output reg Q;
```

```
output Qnot;
```

```
always @ (posedge clk, posedge clr, posedge pre)
```

```
begin
```

```
    //first look at asynchronous inputs
```

```
    if (clr==1'b1)
```

```
    begin
```

```
        Q<=1'b0;
```

```
    end
```

```
    else if (pre==1'b1)
```

```
    begin
```

```
        Q<=1'b1;
```

```
    end
```

```
    else
```

```
    begin
```

```
        Q<=D;
```

```
    end
```

```
end
```

```
assign Qnot=~Q;
```

```
endmodule
```

## Shift Registers

- Type
  - Free-running
  - Universal

Behavior (on active clock edge)

-If asynchronous clear is true,

Register is loaded with zeros

-If asynchronous load is true and clear is false, //parallel load

Register is loaded from the data inputs


-If asynchronous load and clear are both false,

Register contents are shifted according to value of Shift control

//Shift control=1 → shift right; Shift control=0 → shift left

-Else ignore asynchronous input values

#### Universal 4-bit shift register

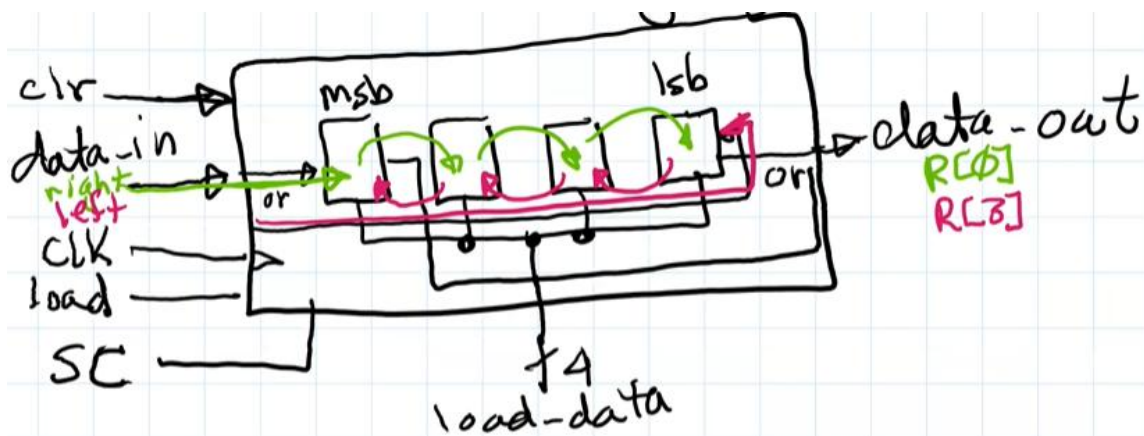

```
module shiftreg (data_in, clk, clr, load, sc, load_data, data_out);
input data_in, clk, clr, load, sc;
input [3:0] load_data;
output data_out;
reg [3:0] R;
always @ (posedge clk, posedge clr, posedge load) //clr and load are asynchronous inputs
begin
    if (clr==1'b1)
    begin
        R<=0;
    end
    else if(load==1'b1)
    begin
        R<=load_data;
    end
    else
    begin
        if(sc==1'b1)//shift right
        begin
            R<={data_in, R[3:1]};
        end
    end
end
```

```

        else//shift left
            begin
                R<={R[2:0],data_in};
            end
        end
    end
end
assign data_out=(sc==1'b1)?R[0]:R[3];
endmodule

-reuse modules with different sized entities
-for 8-bit→replace 3 with 7 and 2 with 6
-for 8-bit→replace 3 with 15 and 2 with 14
//each change to the module, need to resynthesize code and implement into a new bit file
module shiftreg (data_in, clk, clr, load, sc, load_data, data_out);
input data_in, clk, clr, load, sc;
input [3:0] load_data;
output data_out;
reg [3:0] R;
always @ (posedge clk, posedge clr, posedge load) //clr and load are asynchronous inputs
begin
    if (clr==1'b1)
        begin
            R<=0;
        end
    else if(load==1'b1)
        begin
            R<=load_data;
        end
    else
        begin
            if(sc==1'b1)//shift right
                begin
                    R<={data_in, R[3:1]};
                end
            else//shift left
                begin
                    R<={R[2:0],data_in};
                end
            end
        end
    end
end
end

```

```
assign data_out=(sc==1'b1)?R[0]:R[3];
```

```
endmodule
```

-single module that can be implement with the designed register width without being resynthesized

-use parameters to set shift register width

-create an n-bit register using a parameter named **width**

```
module shiftreg (data_in, clk, clr, load, sc, load_data, data_out);
```

```
parameter width=4;//by default shift register is 4-bits wide
```

```
input data_in, clk, clr, load, sc;
```

```
input [(width-1):0] load_data;
```

```
output data_out;
```

```
reg [(width-1):0] R;
```

```
always @ (posedge clk, posedge clr, posedge load) //clr and load are asynchronous inputs
```

```
begin
```

```
    if (clr==1'b1)
```

```
    begin
```

```
        R<=0;
```

```
    end
```

```
    else if(load==1'b1)
```

```
    begin
```

```
        R<=load_data;
```

```
    end
```

```
    else
```

```
    begin
```

```
        if(sc==1'b1)//shift right
```

```
        begin
```

```
            R<={data_in, R[(width-1):1]};
```

```
        end
```

```
        else//shift left
```

```
        begin
```

```
            R<={R[(width-2):0],data_in};
```

```
        end
```

```
    end
```

```
end
```

```
assign data_out=(sc==1'b1)?R[0]:R[(width-1)];
```

```
endmodule
```

-creating an instance of a parameterized module//module top with 4-bit shift register

```
module top(...);
```

```
...
```

```
wire din, clk, clr, ld, sc, dout;
```

```

wire [3:0] data;

shiftreg U1 (.data_in(data_in), .clk(clk), .clr(clr), .load(ld), .sc(sc), ,load_data(data), .data_out(dout));
...
endmodule

-creating an instance of a parameterized module//module top with 32-bit shift register

module top(...);
...
wire din, clk, clr, ld, sc, dout;

wire [31:0] data;

shiftreg #(.width(32)) U1 (.data_in(data_in), .clk(clk), .clr(clr), .load(ld), .sc(sc), ,load_data(data), .data_out(dout));
...
endmodule


```

## Counters

- Counter types
  - Up/Down
  - Modulo N counter
- BCD (Binary Coded Decimal)
- Ring counter
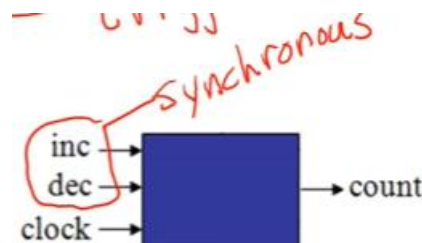
## Binary Up/Down Counters

- Behavior (on active clock edge//positive edge triggered)
  - If inc is true, //increment 增量
    - count = count + 1 on clock edge
  - If dec is true, //decrement 减量
    - count = count - 1 on clock edge
  - If both inc and dec are true,
    - count = count
  - If both inc and dec are false,
    - count = 0



-make a parasitized module that is 8-bit wide by default

### Binary Up/Down Counter

```

module UpDownCnt (clk, dec, inc, count);
parameter width=8;
input clk, inc, dec;
output reg [width-1:0] count;
always @ (posedge clk)
begin
  case({inc, dec})

```

```

2'b00: count<=0;
2'b01: count<=count-1;
2'b10: count<=count+1;
2'b11: count<=count; //is it necessary to use <= instead of =?

```

endcase

end

endmodule

## Modulo N Counter

- Behavior (on active clock edge)

-If count < N-1,

- count = count + 1

-If count == N-1

- count = 0

//Module-N counter

```
module ModNCounter (clk, count, N);
```

```
parameter width;
```

```
input clk;
```

```
input [width-1:0] N; //actually width of N is log2(N)
```

```
output reg [width-1:0] count;
```

```
always @ (posedge clk)
```

```
begin
```

```
  if(count<N-1)
```

```
  begin
```

```
    count<=count+1;
```

```
  end
```

```
  else if (count==N-1)
```

```
  begin
```

```
    count<=0;//recycle count
```

```
  end
```

```
end
```

```
endmodule
```




## Ring Counter

- Behavior

-Q[n-1:0] preset with pattern (ex: 0001)

-On active edge of clock


- Q[n-2:0] = Q[n-1:1]
- Q[n-1] = Q[0]

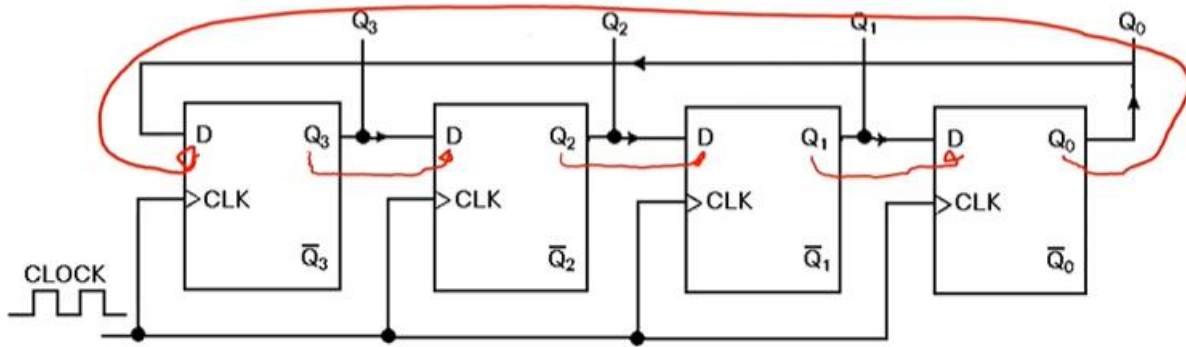


```

module ring(clk, pre, Q);
input clk, pre;
output reg [3:0] Q;
always @ (posedge clk, posedge pre)
begin
    if(pre==1'b1)
    begin
        Q<=4'b1110;
    end
    else
    begin
        Q[3]<=Q[0];
        Q[2:0]<=Q[3:1]; //these two lines can be Q<={Q[0]:Q[3:1]};
    end
end
end
endmodule



```

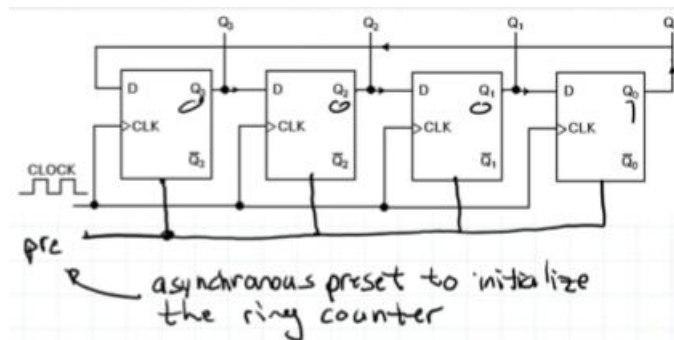

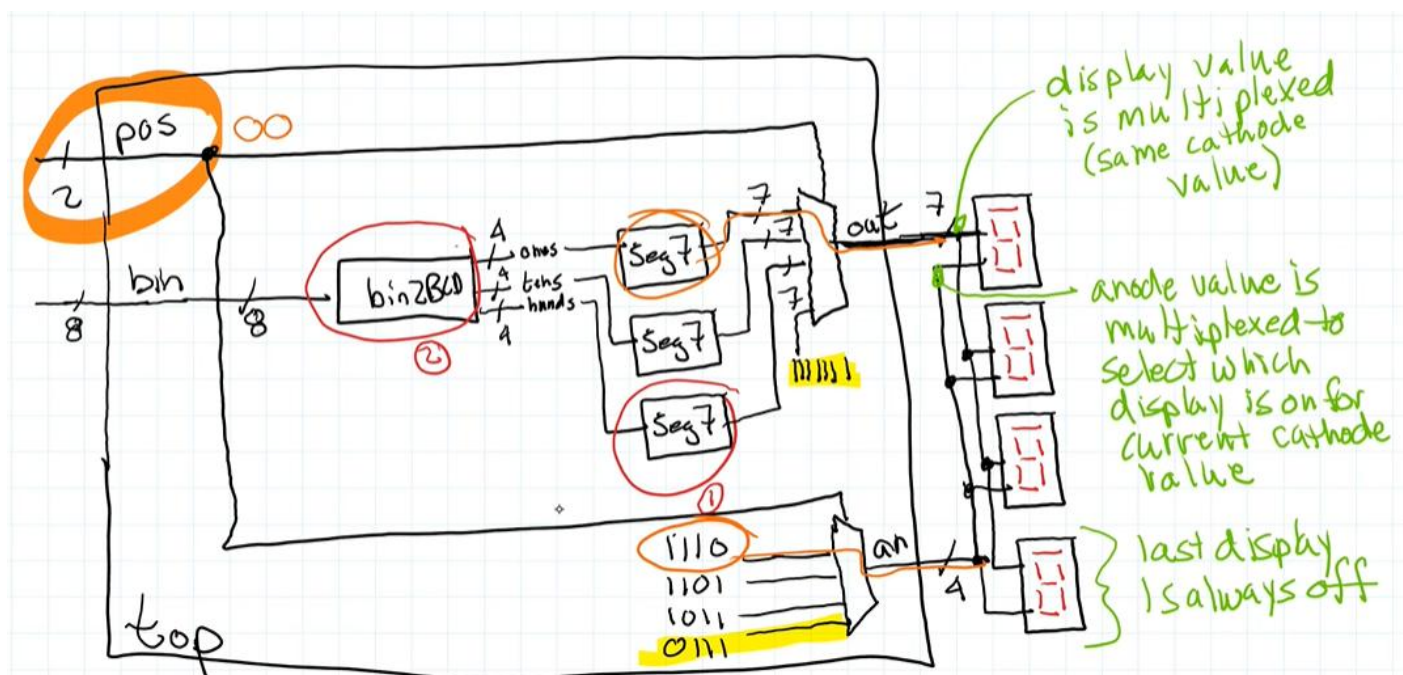The Basys 3 board includes a single 100 MHz oscillator connected to pin W5 (W5 is a MRCC input on bank 34).





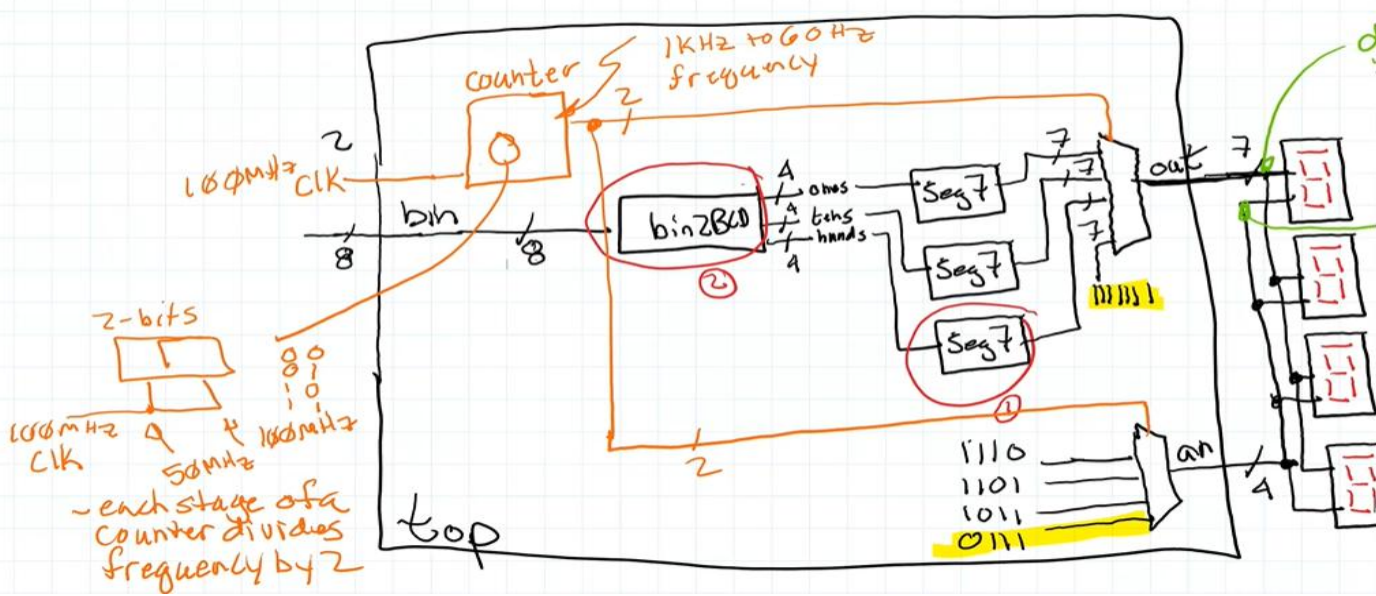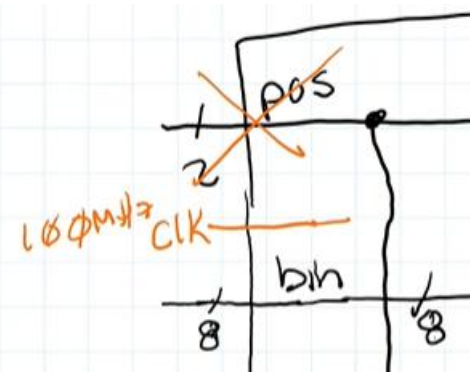

This circuit drives the anode signals and corresponding cathode patterns of each digit in a repeating, continuous succession at an update rate that is faster than the human eye can detect.

For each of the four digits to appear bright and continuously illuminated, all four digits should be driven once every 1 to 16ms, for a refresh frequency of about 1 KHz to 60Hz.

```

CODE:
module Bin8ToBCD(clk, bin, out, an);
input clk;
input [7:0] bin;
output reg [6:0] out;
output reg [3:0] an;
reg [19:0] count; //20-bit counter to divide 100 MHz clock frequency for selecting 7-segment display
wire [1:0] pos;
wire [3:0] ones, tens, hunds;
wire [6:0] seg7ones, seg7tens, seg7hunds;
bin2BCD U1 (.bin(bin), .ones(ones), .tens(tens), .hunds(hunds));
Seg7 U2 (.BCD(ones),.out(seg7ones));
Seg7 U3 (.BCD(tens),.out(seg7tens));
Seg7 U4 (.BCD(hunds),.out(seg7hunds));
always @(posedge clk) //create a 20-bit free running binary counter
begin

```

```

    count<=count+1;
end
assign pos=count[19:18]; //use upper 2-bit of counter for mux select input, too fast would not show clear and too slow would
blink
always @ (pos,seg7ones, seg7tens, seg7hunds)
begin
    //implement mux for 7 segment display
    case(pos)
        2'b00://ones
            begin
                out=seg7ones;
                an=4'b1110;
            end
        2'b01://tens
            begin
                out=seg7tens;
                an=4'b1101;
            end
        2'b10://hunds
            begin
                out=seg7hunds;
                an=4'b1011;
            end
        2'b11://thousands
            begin
                out=7'b1111111;
                an=4'b0111;
            end
    endcase
end
endmodule

module bin2BCD(bin, ones, tens, hunds);
input [7:0] bin;
output [3:0] ones, tens, hunds;
reg [19:0] temp; //temporary register to hold 8-bit binary input and BCD output during shifting and add 3 process
integer cnt; //control variable for the for loop
always @ (bin)
begin
    temp={12'b0, bin}; //concatenate 12 bits of 0 with binary input and store to temp register
    //perform the shift and add 3 algorithm 8 times

```

```

for (cnt=0; cnt<8; cnt=cnt+1)
begin
    temp = temp << 1;//shift temp register to left by 1
    if(cnt<7)//first shifts
    begin
        //test each BCD output >=5
        if(temp[11:8]>=5)//if ones digit >=5
        begin
            temp[11:8]=temp[11:8]+3;
        end
        if(temp[15:12]>=5)//if tens digit >=5
        begin
            temp[15:12]=temp[15:12]+3;
        end
        if(temp[19:16]>=5)//if hunds digit >=5
        begin
            temp[19:16]=temp[19:16]+3;
        end
    end
end
end

assign ones=temp[11:8];
assign tens=temp[15:12];
assign hunds=temp[19:16];

endmodule

module Seg7 (BCD, out);
input [3:0] BCD;
output reg [6:0] out;
always @ (BCD)
begin
    case(BCD) //care about the lsb and msb
        4'b0000:out=7'b1000000;
        4'b0001:out=7'b1111001;
        4'b0010:out=7'b0100100;
        4'b0011:out=7'b0110000;
        4'b0100:out=7'b0011001;
        4'b0101:out=7'b0010010;
        4'b0110:out=7'b0000010;
        4'b0111:out=7'b1111000;
        4'b1000:out=7'b0000000;
    endcase
end

```

```
4'b1001:out=7'b0010000;
```

```
default: out=7'b1111111; //turn off display if invalid number
```


```
endcase
```

```
end
```

```
endmodule
```

## Linear Feedback Shift Register

- Behavior:

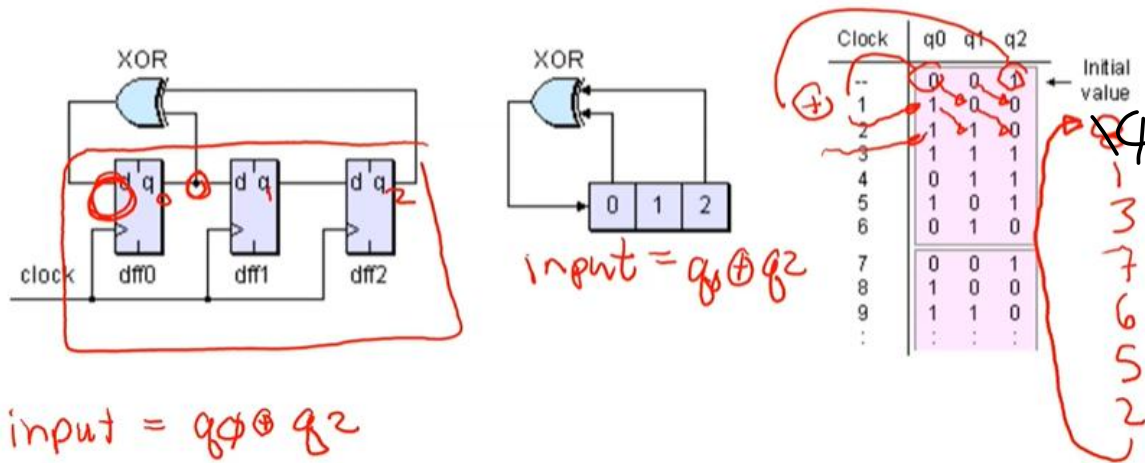


-linear function typically using XOR or XNOR

-deterministic operations

-sequence of values is determined by its current state

-there are a finite number of possible states, the pattern is repeating

-( $2^n$ )-1 is states for an n-bit LFSR

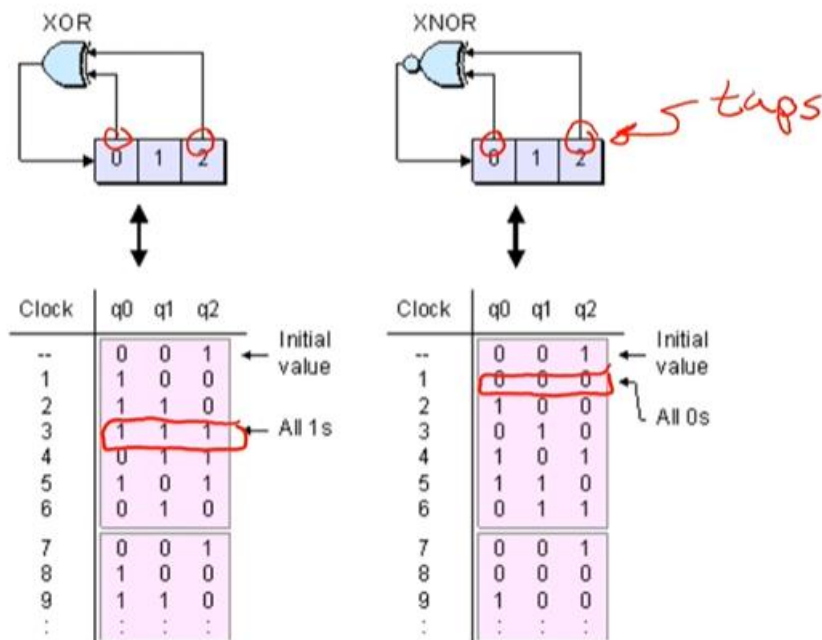

-why use?

-counter


-non-binary count sequence

-very efficient ... think fast

- pseudo random number generator //pseudo:伪装
- pseudo-noise sequence generator
- stream-cipher for cryptography//流密码加密

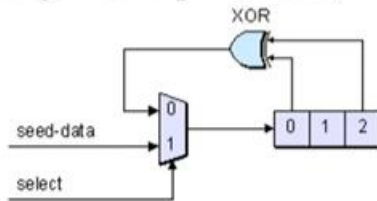
## • Example:

- Create an n-bit LFSR
  - Where  $3 \leq n \leq 16$
- Must create module with
  - Clock and an asynchronous enable input
  - Seed input (n-bits) with synchronous seed input
  - Repeat flag output (pulse at  $2^n-1$ )
  - Shift register output (n-bits)




# of Bits	Length of Loop	Taps
2	3 *	[0,1]
3	7 *	[0,2]
4	15	[0,3]
5	31 *	[1,4]
6	63	[0,5]
7	127 *	[0,6]
8	255	[1,2,3,7]
9	511	[3,8]
10	1,023	[2,9]
11	2,047	[1,10]
12	4,095	[0,3,5,11]
13	8,191 *	[0,2,3,12]
14	16,383	[0,2,4,13]
15	32,767	[0,14]
16	65,535	[1,2,4,15]
17	131,071	[2,16]
18	262,143	[6,17]
19	524,287 *	[0,1,4,18]
20	1,048,575	[2,19]
21	2,097,151	[1,20]
22	4,194,303	[0,21]
23	8,388,607	[4,22]
24	16,777,215	[0,2,3,23]
25	33,554,431	[2,24]
26	67,108,863	[0,1,5,25]
27	134,217,727	[0,1,4,26]
28	268,435,455	[2,27]
29	536,870,911	[1,28]
30	1,073,741,823	[0,3,5,29]
31	2,147,483,647 *	[2,30]
32	4,294,967,295	[1,5,6,31]



//LFSR example:

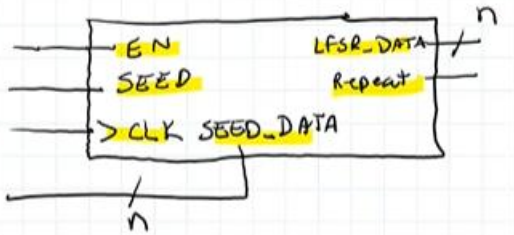

- SEED\_DATA = initial value

# of Bits	Length of Loop	Taps
2	3 *	[0,1]
3	7 *	[0,2]
4	15	[0,3]
5	31 *	[1,4]
6	63	[0,5]
7	127 *	[0,6]
8	255	[1,2,3,7]
9	511	[3,8]
10	1,023	[2,9]
11	2,047	[1,10]
12	4,095	[0,3,5,11]
13	8,191 *	[0,2,3,12]
14	16,383	[0,2,4,13]
15	32,767	[0,14]
16	65,535	[1,2,4,15]

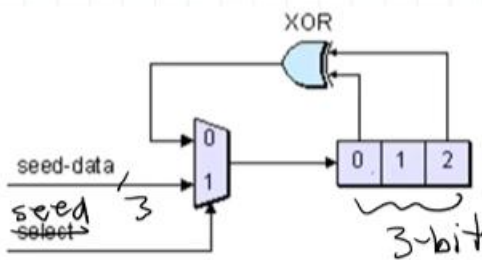

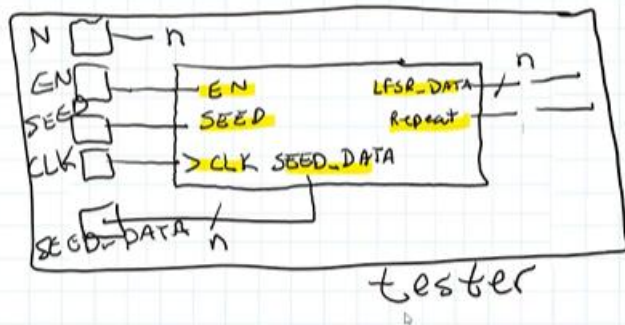 

Verilog:

```

module LFSR(clk, en, seed, seed_data, LFSR_data, Repeat);
parameter n=4; //default width of LFSR is 4-bit
input clk, en, seed;
input [n-1:0] seed_data;
output Repeat;
output [n-1:0] LFSR_data;

reg [n-1:0] LFSR;
reg XOR; //output from linear function

always @ (posedge clk, posedge en)
begin
    if(en==1'b1)//LFSR is enabled
    begin
        if(seed==1'b1)//seeding the LFSR
        begin
            LFSR<=seed_data;//parallel load the LFSR register
        end
        else//not seeding, just shifting
        begin
            LFSR<={LFSR[n-1:0],XOR};//shift LFSR with linear function (XOR) output
        end
    end
end

```

```

        end
    end
    else //LFSR is not enabled
    begin
        LFSR<=0;//clear LFSR when not enabled
    end
end

//create the linear function for feedback of XOR value
always @*
begin
    case(n)
        3:XOR=LFSR[0]^LFSR[2];
        4:XOR=LFSR[0]^LFSR[3];
        5:XOR=LFSR[1]^LFSR[4];
        6:XOR=LFSR[0]^LFSR[5];
        7:XOR=LFSR[0]^LFSR[6];
        8:XOR=LFSR[1]^LFSR[2]^LFSR[3]^LFSR[7];
        9:XOR=LFSR[3]^LFSR[8];
        10:XOR=LFSR[2]^LFSR[9];
        11:XOR=LFSR[1]^LFSR[10];
        12:XOR=LFSR[0]^LFSR[3]^LFSR[5]^LFSR[11];
        13:XOR=LFSR[0]^LFSR[2]^LFSR[3]^LFSR[12];
        14:XOR=LFSR[0]^LFSR[2]^LFSR[4]^LFSR[13];
        15:XOR=LFSR[0]^LFSR[14];
        16:XOR=LFSR[1]^LFSR[2]^LFSR[4]^LFSR[15];
    endcase
end

assign LFSR_data=LFSR;

assign Repeat={LFSR==seed_data}?1'b1:1'b0;//set Repeat to 1 whenever LFSR register equals the initial seed data (repeats)
endmodule

testbench:
module Tester();
parameter N=3;
reg CLK, EN, SEED;
reg [N-1:0] SEED_DATA;
wire [N-1:0] LFSR_DATA;
wire REPEAT;

```

```
//create n 8-bit LFSR instance
```

```
LFSR                                                                    #(.n(N))
UUT(.clk(CLK), .en(EN), .seed(SEED), .seed_data(SEED_DATA), .LFSR_data(LFSR_DATA), .Repeat(REPEAT));
initial
begin
    CLK=0;
    EN=0;
    SEED=0;
    SEED_DATA=3'b100;
    #10;
    EN=1;
    SEED=1;
    #20;
    SEED=0;
end

always
begin
    #5;
    CLK=~CLK;
end

endmodule
```

## FSM Design with Verilog

### Mealy & Moore Machines

- Mealy modeled machines

- The next state and output is determined by current state of the machine and current input to the machine

- Next State = F(current state, input)

- Output = G(current state, input)


- Moore modeled machines

- The next output is only determined by the current state and not directly on the current input

- Next State = F(current state, input)


- Output = G(current state)



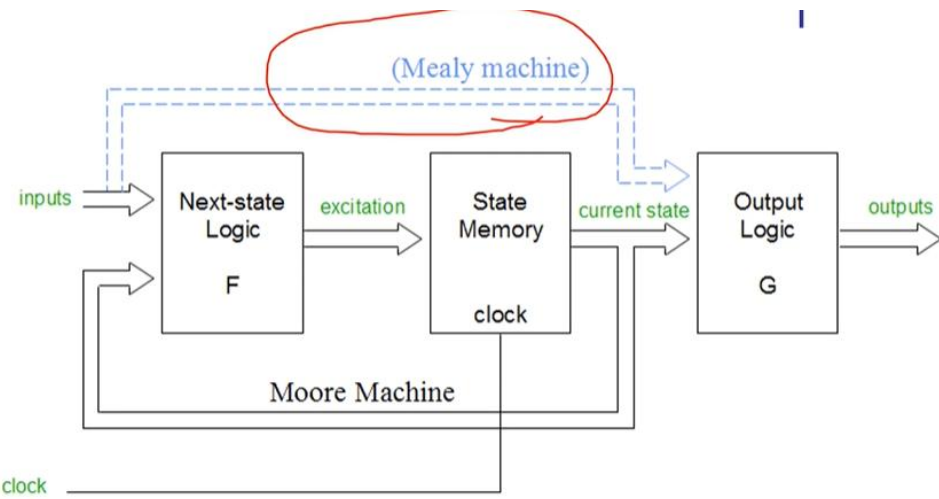
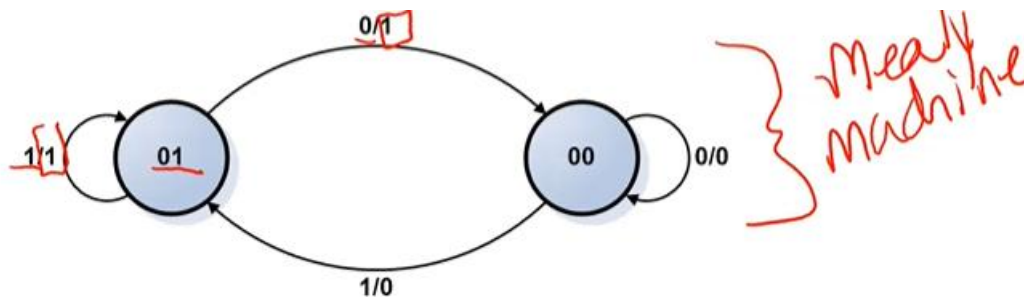
## State Diagrams

- Graphical representation of sequential circuit operation captured in state table
  - State represented by a circle with corresponding number of the state
  - Transitions between states indicated by directed lines (arcs) connecting the circles
- Numbered as “input x / output y” associated with transition



## Verilog State Machines

- We need registers to hold
  - the current state
  - always @(posedge clk) block
- We need next state function
  - Where do we go from each state given the inputs
  - State by state case analysis
    - Next state determined by current state and inputs
- We need the output function
  - State by state analysis
    - Moore: output determined by current state only
    - Mealy: output determined by current state and inputs
- State register
  - Declare two values
    - state : current state – output of state register
    - nxtState : next state – input to state register
  - We rely on next state function to give us nxtState

-Declare symbols for states with state assignment

```
localparam IDLE=0, WAITFORB=1, } constant values
      DONE=2, ERROR=3;          for each state
```

```
reg [1:0] state, // Current state
      nxtState; // Next state
```

2-bit registers

## • Next State Function

-Combinational logic function

- Inputs : state, inputs
- Output : nxtState

-We could use assign statements

-We will use an always @(\*) block instead // \* means continue

- Allows us to use procedural block statements like “if” and “case”


-Describes what happens in each state (typically use case statement)

## • Next State Function (cont.)

```
always @(*) begin
  nxtState = state; // Default next state: don't move
  case (state)
    IDLE : begin
      if (B) nxtState = ERROR;
      else if (A) nxtState = WAITFORB;
    end
    WAITFORB : begin
      if (B) nxtState = DONE;
    end
    DONE : begin
    end
    ERROR : begin
    end
  endcase
end
```

else // A=0, B=0  
nxtState = IDLE;

inputs A, B

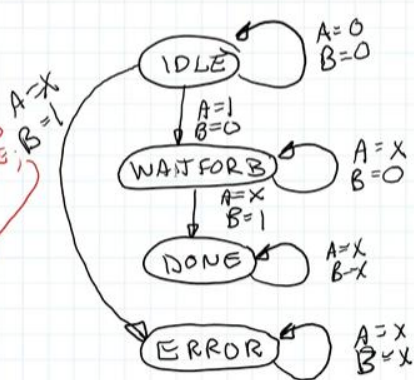


## • Output Function

-Describe the output of each state

-Typically combined with next state function

```
always @(*) begin
  nxtState = state; // Default next state: stay where we are
  out = 0; // Default output
  case (state)
    IDLE : begin
      if (B) nxtState = ERROR;
      else if (A) nxtState = WAITFORB;
    end
    WAITFORB : begin
      if (B) nxtState = DONE;
    end
    DONE : begin
      out = 1;
    end
    ERROR : begin
    end
  endcase
end
```

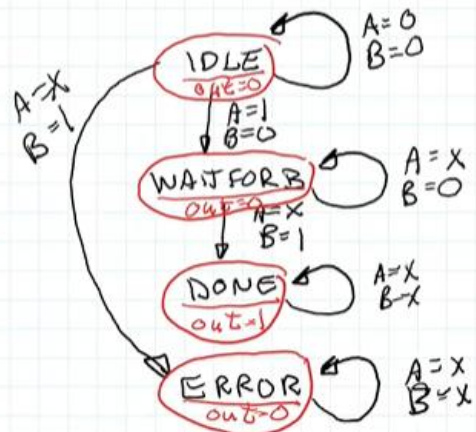Moore machine,  
output only dependent  
on current state





# Design of FSM Circuits

-edge detected
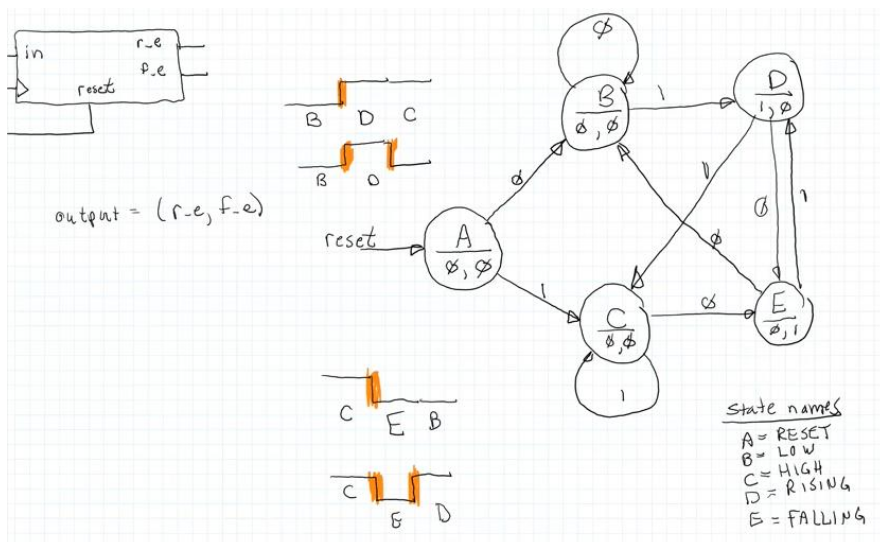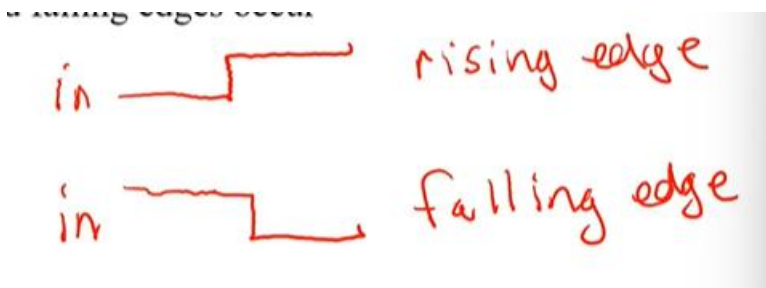
## • Example:

-Moore edge detection state machine

- Read continuous logic level input signal, and determine when rising and falling edges occur



-state registers

-state

-next state

-5 states → 3-bits

```
module MooreEdgeDetect(clk, in, reset, f_e, r_e);
```

```
localparam RESET=0, LOW=1, HIGH=2, RISING=3, FALLING=4; //or change it to parameter and upon the module
```

```
input clk, in, reset;
```

```
output reg f_e, r_e;
```

```
reg [2:0] state, nextstate;
```

```
always @ (posedge clk)
```

```
begin
```

```
if(reset==1'b1)
```

```
begin
```

```
state<=RESET;
```

```
end
```

```
else
```

```
begin
```

```

        state<=nextstate;
    end
end

always @ (*)//next state and output functions
begin
    nextstate=state;//default set next state to current state
    r_e=1'b0;
    f_e=1'b0;

    case(state)
        RESET:begin
            if (in==1'b0)
                begin
                    nextstate<=LOW;
                end
            else
                begin
                    nextstate<=HIGH;
                end
            end
        LOW:begin
            if (in==1'b1)
                begin
                    nextstate<=RISING;
                end
            end
        HIGH:begin
            if (in==1'b0)
                begin
                    nextstate<=FALLING;
                end
            end
        RISING:begin
            r_e=1'b1; //set the rising edge flag to 1
            if (in==1'b0)
                begin
                    nextstate<=FALLING;
                end
            else

```

```


begin
    nextstate<=HIGH;
end
end
FALLING:begin
    f_e=1'b1; //set the falling edge flag to 1
    if (in==1'b0)
    begin
        nextstate<=LOW;
    end
    else
    begin
        nextstate<=RISING;
    end
    end
end
default:begin
    nextstate=RESET;
end
endcase
end
endmodule

```

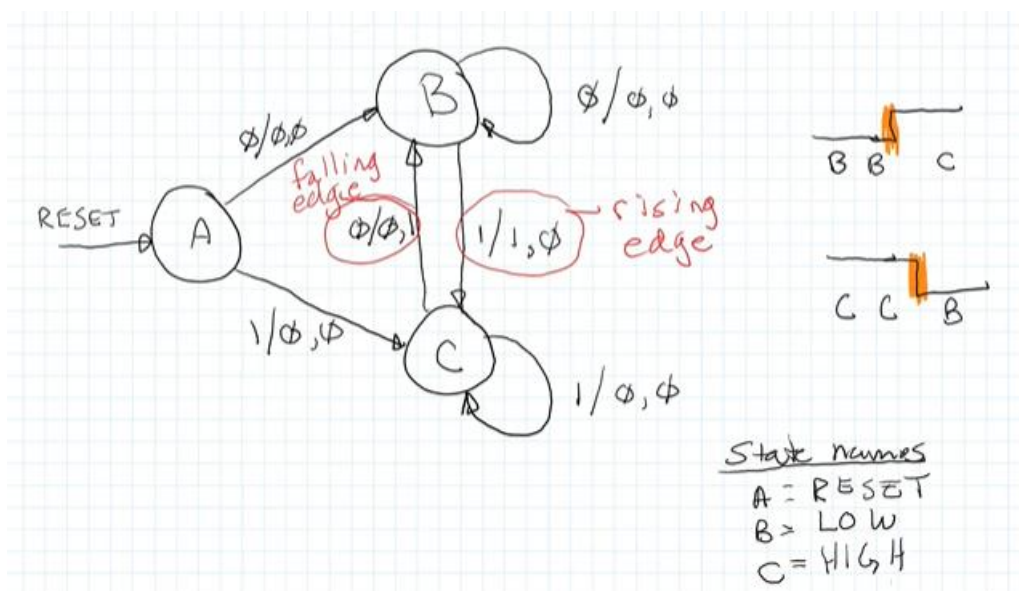• Example:

-Mealy edge detection state machine

- Read continuous logic level input signal, and determine when rising and falling edges occur



```

module MealyEdgeDetect(clk, in, reset, f_e, r_e);

```

```

    localparam RESET=0, LOW=1, HIGH=2; //or change it to parameter and upon the module

```

```

    input clk, in, reset;

```

```
output reg f_e, r_e;
```

```
reg [1:0] state, nextstate;
```

```
always @ (posedge clk)
```

```
begin
```

```
    if(reset==1'b1)
```

```
    begin
```

```
        state<=RESET;
```

```
    end
```

```
    else
```

```
    begin
```

```
        state<=nextstate;
```

```
    end
```

```
end
```

```
always @ (*)//next state and output functions
```

```
begin
```

```
    nextstate=state;//default set next state to current state
```

```
    r_e=1'b0;
```

```
    f_e=1'b0;
```

```
    case(state)
```

```
        RESET:begin
```

```
            if (in==1'b0)
```

```
            begin
```

```
                nextstate<=LOW;
```

```
            end
```

```
            else
```

```
            begin
```

```
                nextstate<=HIGH;
```

```
            end
```

```
        end
```

```
        LOW:begin
```

```
            if (in==1'b1)
```

```
            begin
```

```
                nextstate<=HIGH;
```

```
                r_e=1'b1; //set rising edge flag
```

```
            end
```

```
        end
```

```
        HIGH:begin
```

```
        if (in==1'b0)
            begin
                nextstate<=LOW;
                f_e=1'b1;
            end
        end
    end

    default:begin
        nextstate=RESET;
    end

endcase
end
endmodule
```

## 3-8 译码器

(1) verilog 程序

```
module decoder_38(A,Y);
input [2:0] A;
output [7:0] Y;

////use assign 数据流
//assign Y[0]=~A[2]&~A[1]&~A[0];
//assign Y[1]=~A[2]&~A[1]&A[0];
//assign Y[2]=~A[2]&A[1]&~A[0];
//assign Y[3]=~A[2]&A[1]&A[0];
//assign Y[4]=A[2]&~A[1]&~A[0];
//assign Y[5]=A[2]&~A[1]&A[0];
//assign Y[6]=A[2]&A[1]&~A[0];
//assign Y[7]=A[2]&A[1]&A[0];

////use for loop 行为级
//reg [7:0] Y;
//integer cnt;
//always @(A)
//begin
//    for(cnt=0; cnt<8; cnt=cnt+1) //set the value for each bit of the output
//        begin
//            if(cnt==A) //check if current bit location equals to the input value
//                begin
//                    Y[cnt]=1'b1;
//                end
//            else
//                begin
//                    Y[cnt]=1'b0;
//                end
//            end
//        end
//    end

////use continuous assignment 数据流建模
//assign Y=8'b0000_0001<<A;

//use case statement with procedural block 行为级建模
reg [7:0] Y;
```



**always @(A)**

**begin**

**case(A)**

**3'b000: Y=8'b0000\_0001;**

**3'b001: Y=8'b0000\_0010;**

**3'b010: Y=8'b0000\_0100;**

**3'b011: Y=8'b0000\_1000;**

**3'b100: Y=8'b0001\_0000;**

**3'b101: Y=8'b0010\_0000;**

**3'b110: Y=8'b0100\_0000;**

**3'b111: Y=8'b1000\_0000;**

**default:Y=8'b0000\_0000;**

**endcase**

**end**

**endmodule**

(2) testbench 程序

**module test38();**

**reg [2:0] a;**

**wire [7:0] y;**

**decoder\_38 uu1 (a,y);**

**initial**

**begin**

**a=3'b000;**

**#10 a=3'b001;**

**#10 a=3'b010;**

**#10 a=3'b011;**

**#10 a=3'b100;**

**#10 a=3'b101;**

**#10 a=3'b110;**


**#10 a=3'b111;**

**#10 \$finish;**

**end**

**endmodule**



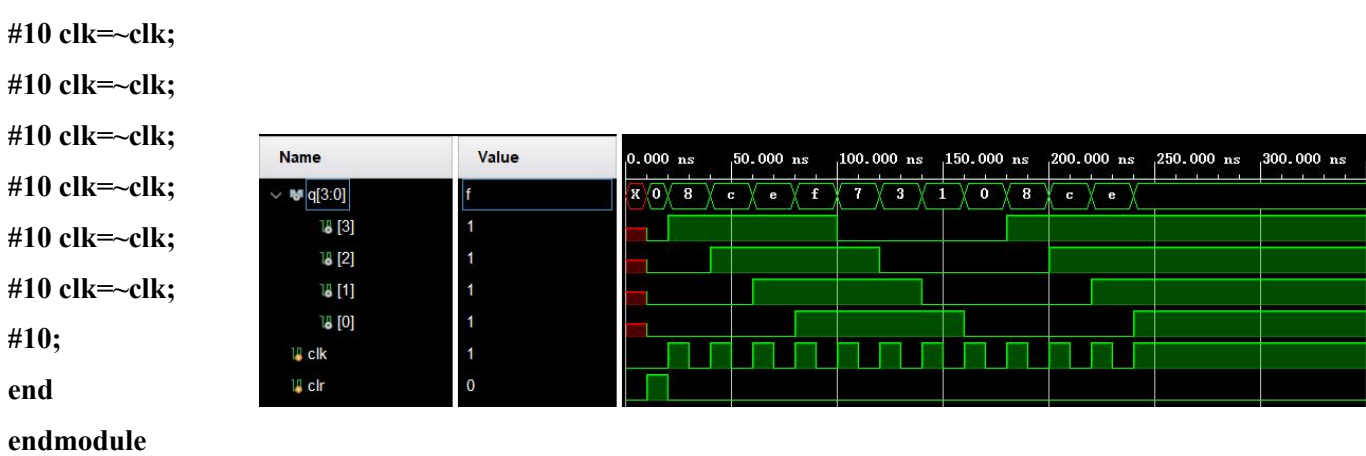

## 4 位移位寄存器

Verilog 程序:

```

module yi4(CLR, CLK, D, DSL, DSR, S, Q);
input CLR, CLK, DSL, DSR;
input [3:0] D;
input [1:0] S;
output reg [3:0] Q;
always @ (posedge CLR or posedge CLK)
    if (CLR)
        Q=4'b0000;
    else
        case (S)
            2'b00: Q<=Q;
            2'b01: Q<={Q[2:0], DSR};
            2'b10: Q<={DSL, Q[3:1]};
            2'b11: Q<=D;
        endcase
endmodule

```

Testbench 程序:

```

module testyi4();
reg clr, clk, dsl, dsr;
reg [3:0] d;
reg [1:0] s;
wire [3:0] q;
yi4 uu1 (. CLR(clr), .CLK(clk), .DSL(dsl), .DSR(dsr), .D(d), .S(s), .Q(q));
initial
begin
    clr=0; clk=0; d=4'b1011; s=2'b00; dsl=1; dsr=0;

```

```

#10 clk=~clk; s=2'b11;

#10 clk=~clk;

#10 clk=~clk; s=2'b10;

#10 clk=~clk;

#10 clk=~clk; s=2'b01;

#10 clk=~clk;

#10 clk=~clk; s=2'b00;

#10 clk=~clk;


#10 clr=1;

#10 $finish;

end

endmodule

```

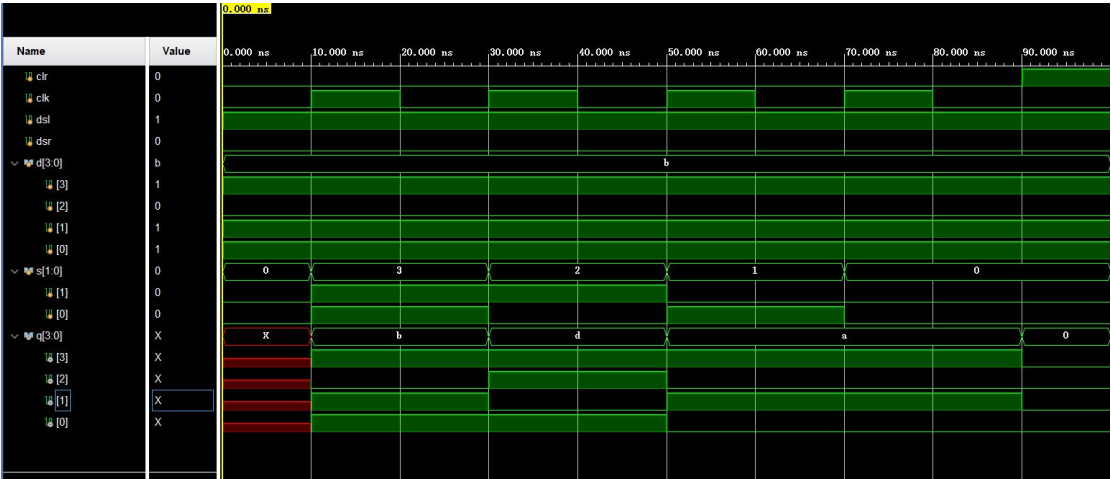

## 四位脉动全加器

Verilog 程序:

```

module rpcounter(CLK, ST, Q);
input CLK, ST;
output [3:0] Q;
Tff tff0(CLK, ST,Q[0]);
Tff tff1(Q[0], ST, Q[1]);
Tff tff2(Q[1], ST, Q[2]);
Tff tff3(Q[2], ST, Q[3]);
endmodule

```

```

module Tff (clk, st, qq);
input clk,st;
output qq;
Dff df (clk, st, ~qq, qq);
endmodule

```

```

module Dff(clock, reset, d, q);
input clock, reset, d;
output reg q;
always @(negedge clock or posedge reset)
  if (reset)
    q=1'b0;
  else
    q<=d;
endmodule

```

## Testbench 程序:

**module rptest();**

```
reg clk, st;
```

```
wire [3:0] q;
```

```
rpcounter rp (clk, st, q);
```

**initial**

**begin**

**clk=0; st=0;**

```
#10 clk=~clk; st=1;
```

```
#10 clk=~clk; st=0;
```

```
#10 clk=~clk;
```

```
#10 clk=~clk;
```

```
#10 clk=~clk;
```

```
#10 clk=~clk;
```

end  
endmodule